

# Solution of ECE 300 Test 7 S11

1. With reference to the circuit below fill in the blanks with numbers.

Before  $t = 0$  the capacitor current is zero. Due to the voltage source alone  $i_1 = i_2 = i_3 = -\frac{10V}{22\Omega + 50\Omega + 35\Omega} = -93.5\text{mA}$

. The three resistor voltages are then  $v_1 = -93.5\text{mA} \times 22\Omega = -2.057\text{ V}$ ,  $v_2 = -93.5\text{mA} \times 50\Omega = -4.675\text{ V}$  and  $v_3 = -93.5\text{ mA} \times 35\Omega = -3.2725\text{ V}$ . The capacitor voltage is  $v_2 + v_3$  and that is  $-7.9475\text{ V}$ . Due to the current source alone  $v_3(t) = 100\text{mA} \times 35\Omega \parallel (50\Omega + 22\Omega) = 2.3551\text{ V}$ ,  $i_3 = 2.3551\text{ V}/35\Omega = 67.3\text{ mA}$

$i_1 = i_2 = -2.3551\text{ V}/(50\Omega + 22\Omega) = -32.7\text{mA}$ ,  $v_1 = -32.7\text{mA} \times 22\Omega = -0.7196\text{ V}$  and  $v_2 = -32.7\text{mA} \times 50\Omega = -1.635\text{ V}$  and  $v_C = -v_1 = 0.7196\text{ V}$ .

At  $t = 0^+$ , due to the voltage source alone the capacitor voltage is still  $-7.9475\text{ V}$  and  $v_s = -2\text{ V}$ . Therefore  $v_1 = 5.9475\text{ V}$ ,  $i_1 = 5.9475 / 22\Omega = 270.3\text{mA}$ ,  $i_2 = i_3 = -7.9475\text{V}/(50\Omega + 35\Omega) = -93.5\text{ mA}$ ,  $v_2 = -4.675\text{ V}$  and  $v_3 = -3.2725\text{ V}$ ,  $i_C = i_1 - i_2 = 270.3\text{mA} - (-93.5\text{mA}) = 363.8\text{mA}$ . Due to the current source alone,  $i_s = 0$ , the capacitor voltage is still  $0.7196\text{ V}$ ,  $i_1 = -v_C / 22\Omega = -32.7\text{ mA}$ ,  $i_2 = i_3 = 0.7196\text{V}/(50\Omega + 35\Omega) = 8.5\text{ mA}$ ,  $v_2 = 8.5\text{mA} \times 50\Omega = 0.4233\text{ V}$  and  $v_3 = 8.5\text{mA} \times 35\Omega = 0.2975\text{ V}$ . The capacitor current is  $i_C = i_1 - i_2 = -32.7\text{mA} - 8.5\text{mA} = -41.2\text{mA}$ .

At  $t \rightarrow \infty$ , capacitor current is again zero, current source is at zero and voltage source is  $-2\text{ V}$ .

$i_1 = i_2 = i_3 = -2\text{V}/(22\Omega + 50\Omega + 35\Omega) = -18.7\text{mA}$ ,  $v_1 = -18.7\text{mA} \times 22\Omega = -0.4122\text{V}$ ,  $v_2 = -18.7\text{mA} \times 50\Omega = -0.935\text{V}$ ,  $v_3 = -18.7\text{mA} \times 35\Omega = -0.6545\text{V}$  and  $v_C = v_2 + v_3 = -1.5895\text{ V}$ .

$$\begin{aligned} v_1(0^-) &= -2.7766\text{ V} & v_2(0^-) &= -6.31\text{ V} & v_3(0^-) &= -0.9174\text{ V} & v_C(0^-) &= -7.2279\text{ V} \\ v_1(0^+) &= 5.2279\text{ V} & v_2(0^+) &= -4.2517\text{ V} & v_3(0^+) &= -2.975\text{ V} & v_C(0^+) &= -7.2279\text{ V} \\ v_1(\infty) &= -0.4122\text{ V} & v_2(\infty) &= -0.935\text{ V} & v_3(\infty) &= -0.6545\text{ V} & v_C(\infty) &= -1.5895\text{ V} \end{aligned}$$


$$\begin{aligned} i_1(0^-) &= -126.2\text{ mA} & i_2(0^-) &= -126.2\text{ mA} & i_3(0^-) &= -26.2\text{ A} & i_C(0^-) &= 0\text{ mA} \\ i_1(0^+) &= 237.6\text{ mA} & i_2(0^+) &= -85\text{ mA} & i_3(0^+) &= -85\text{ mA} & i_C(0^+) &= 322.6\text{ mA} \\ i_1(\infty) &= -18.7\text{ mA} & i_2(\infty) &= -18.7\text{ mA} & i_3(\infty) &= -18.7\text{ mA} & i_C(\infty) &= 0\text{ mA} \end{aligned}$$

The time constant is  $\tau = 15\mu\text{F} \times 22\Omega \parallel (50\Omega + 35\Omega) = 0.2622\text{ms}$ .

$$\begin{aligned} i_1(t) &= [-66.3\text{mA}e^{-t/\tau} + i_1(\infty)], t > 0 & i_C(t) &= [322.6\text{mA}e^{-t/\tau} + i_C(\infty)], t > 0 \\ v_3(t) &= [-2.3205\text{V}e^{-t/\tau} + v_3(\infty)], t > 0 & v_C(t) &= [-5.6384\text{V}e^{-t/\tau} + v_C(\infty)], t > 0 \end{aligned}$$

$$v_s(t) = -10 + 8u(t)\text{ V}, i_s(t) = 100u(-t)\text{ mA}, R_1 = 22\Omega$$
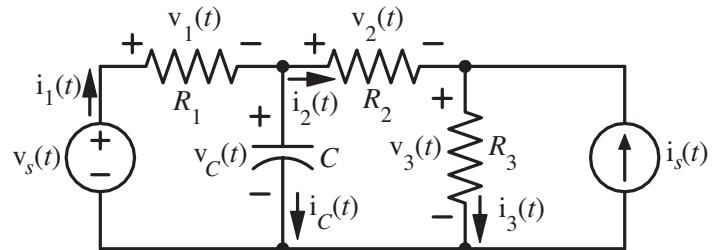
$$R_2 = 50\Omega, R_3 = 35\Omega, C = 15\mu\text{F}$$



# Solution of ECE 300 Test 7 S11

1. With reference to the circuit below fill in the blanks with numbers.

Before  $t = 0$  the capacitor current is zero. Due to the voltage source alone  $i_1 = i_2 = i_3 = \frac{10V}{22\Omega + 50\Omega + 35\Omega} = 93.5 \text{ mA}$ .

The three resistor voltages are then  $v_1 = 93.5\text{mA} \times 22\Omega = 2.057 \text{ V}$ ,  $v_2 = 93.5\text{mA} \times 50\Omega = 4.675 \text{ V}$  and  $v_3 = 93.5 \text{ mA} \times 35\Omega = 3.2725 \text{ V}$ . The capacitor voltage is  $v_2 + v_3$  and that is  $7.9475 \text{ V}$ . Due to the current source alone  $v_3(t) = 200\text{mA} \times 35\Omega \parallel (50\Omega + 22\Omega) = 4.71 \text{ V}$ ,  $i_3 = 4.71\text{V}/35\Omega = 134.6 \text{ mA}$   $i_1 = i_2 = -4.71 \text{ V}/(50\Omega + 22\Omega) = -65.4\text{mA}$ ,  $v_1 = -65.4\text{mA} \times 22\Omega = -1.4392 \text{ V}$  and  $v_2 = -65.4\text{mA} \times 50\Omega = -3.27 \text{ V}$  and  $v_C = -v_1 = 1.4392 \text{ V}$ .

At  $t = 0^+$ , due to the voltage source alone the capacitor voltage is still  $7.9475 \text{ V}$  and  $v_s = 2 \text{ V}$ . Therefore  $v_1 = -5.9475 \text{ V}$ ,  $i_1 = -5.9475 / 22\Omega = -270.3\text{mA}$ ,  $i_2 = i_3 = 7.9475\text{V}/(50\Omega + 35\Omega) = 93.5 \text{ mA}$ ,  $v_2 = 4.675 \text{ V}$  and  $v_3 = 3.2725 \text{ V}$ ,  $i_C = i_1 - i_2 = -270.3\text{mA} - (93.5\text{mA}) = -363.8\text{mA}$ . Due to the current source alone,  $i_s = 0$ , the capacitor voltage is still  $1.4392 \text{ V}$ ,  $i_1 = -v_C / 22\Omega = -65.4 \text{ mA}$ ,  $i_2 = i_3 = 1.4392\text{V}/(50\Omega + 35\Omega) = 17 \text{ mA}$ ,  $v_2 = 17\text{mA} \times 50\Omega = 0.8466 \text{ V}$  and  $v_3 = 17\text{mA} \times 35\Omega = 0.595 \text{ V}$ . The capacitor current is  $i_C = i_1 - i_2 = -65.4\text{mA} - 17\text{mA} = -82.4\text{mA}$ .

At  $t \rightarrow \infty$ , capacitor current is again zero, current source is at zero and voltage source is  $2 \text{ V}$ .  
 $i_1 = i_2 = i_3 = 2\text{V}/(22\Omega + 50\Omega + 35\Omega) = 18.7\text{mA}$ ,  $v_1 = 18.7\text{mA} \times 22\Omega = 0.4122\text{V}$ ,  $v_2 = 18.7\text{mA} \times 50\Omega = 0.935\text{V}$ ,  
 $v_3 = 18.7\text{mA} \times 35\Omega = 0.6545\text{V}$  and  $v_C = v_2 + v_3 = 1.5895 \text{ V}$ .

$$\begin{aligned} v_1(0^-) &= 0.618 \text{ V} & v_2(0^-) &= 1.405 \text{ V} & v_3(0^-) &= 7.9825 \text{ V} & v_C(0^-) &= 9.3867 \text{ V} \\ v_1(0^+) &= -7.3867 \text{ V} & v_2(0^+) &= 5.5216 \text{ V} & v_3(0^+) &= 3.8675 \text{ V} & v_C(0^+) &= 9.3867 \text{ V} \\ v_1(\infty) &= 0.4122 \text{ V} & v_2(\infty) &= 0.935 \text{ V} & v_3(\infty) &= 0.6545 \text{ V} & v_C(\infty) &= 1.5895 \text{ V} \end{aligned}$$

$$\begin{aligned} i_1(0^-) &= 28.1 \text{ mA} & i_2(0^-) &= 28.1 \text{ mA} & i_3(0^-) &= 228.1 \text{ A} & i_C(0^-) &= 0 \text{ mA} \\ i_1(0^+) &= -335.7 \text{ mA} & i_2(0^+) &= 110.5 \text{ mA} & i_3(0^+) &= 110.5 \text{ mA} & i_C(0^+) &= -446.2 \text{ mA} \\ i_1(\infty) &= 18.7 \text{ mA} & i_2(\infty) &= 18.7 \text{ mA} & i_3(\infty) &= 18.7 \text{ mA} & i_C(\infty) &= 0 \text{ mA} \end{aligned}$$

The time constant is  $\tau = 15\mu\text{F} \times 22\Omega \parallel (50\Omega + 35\Omega) = 0.2622\text{ms}$ .

$$\begin{aligned} i_3(t) &= [91.8\text{mA}e^{-t/\tau} + i_3(\infty)], t > 0 & i_C(t) &= [-446.2\text{mA}e^{-t/\tau} + i_C(\infty)], t > 0 \\ v_3(t) &= [3.213\text{V}e^{-t/\tau} + v_3(\infty)], t > 0 & v_C(t) &= [7.7972\text{V}e^{-t/\tau} + v_C(\infty)], t > 0 \end{aligned}$$

$$\begin{aligned} v_s(t) &= 10 - 8u(t) \text{ V}, i_s(t) = 200u(-t) \text{ mA}, R_1 = 22\Omega \\ R_2 &= 50\Omega, R_3 = 35\Omega, C = 15\mu\text{F} \end{aligned}$$

