

Solution of ECE 300 Test 7 F11

1. Fill in the blanks with numbers.

$$v_1(0^-) = \text{_____} \text{ V} \quad v_2(0^-) = \text{_____} \text{ V} \quad v_L(0^-) = \text{_____} \text{ V}$$


$$v_1(0^+) = \text{_____} \text{ V} \quad v_2(0^+) = \text{_____} \text{ V} \quad v_L(0^+) = \text{_____} \text{ V}$$

$$i_1(0^-) = \text{_____} \text{ A} \quad i_L(0^-) = \text{_____} \text{ A}$$

$$i_1(0^+) = \text{_____} \text{ A} \quad i_L(0^+) = \text{_____} \text{ A}$$

$$\tau = \text{_____} \text{ ms}$$
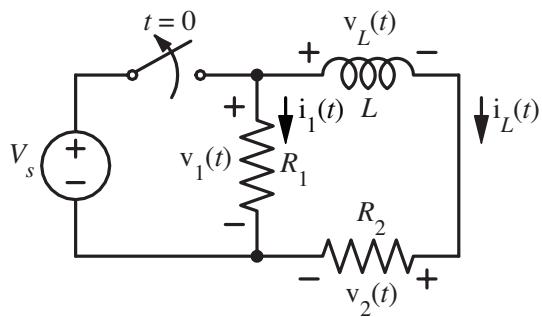
$$V_s = 14 \text{ V}, R_1 = 9 \Omega, R_2 = 20 \Omega, L = 150 \text{ mH}$$



$$v_1(0^-) = V_s = 14 \text{ V} \quad v_2(0^-) = V_s = 14 \text{ V} \quad v_L(0^-) = 0 \text{ V}$$

$$v_1(0^+) = i_1(0^+) \times R_1 = -6.3 \text{ V} \quad v_2(0^+) = i_L(0^+) \times R_2 = 14 \text{ V} \quad v_L(0^+) = v_1(0^+) - v_2(0^+) = -20.3 \text{ V}$$

$$i_1(0^-) = V_s / R_1 = 14 / 9 = 1.556 \text{ A} \quad i_L(0^-) = V_s / R_2 = 14 / 20 = 0.7 \text{ A}$$

$$i_1(0^+) = -i_L(0^+) = -0.7 \text{ A} \quad i_L(0^+) = i_L(0^-) = 0.7 \text{ A}$$

$$\tau = L / R_{eq} = 0.15 / 29 = 5.17 \text{ ms}$$


2. Fill in the blanks with numbers.

$$\begin{aligned} i_1(0^-) &= \text{_____ A} & i_2(0^-) &= \text{_____ A} & i_3(0^-) &= \text{_____ A} & i_c(0^-) &= \text{_____ A} \\ i_1(0^+) &= \text{_____ A} & i_2(0^+) &= \text{_____ A} & i_3(0^+) &= \text{_____ A} & i_c(0^+) &= \text{_____ A} \\ i_1(\infty) &= \text{_____ A} & i_2(\infty) &= \text{_____ A} & i_3(\infty) &= \text{_____ A} & i_c(\infty) &= \text{_____ A} \end{aligned}$$

$$\begin{aligned} v_1(0^-) &= \text{_____ V} & v_2(0^-) &= \text{_____ V} & v_c(0^-) &= \text{_____ V} & v_i(0^-) &= \text{_____ V} \\ v_1(0^+) &= \text{_____ V} & v_2(0^+) &= \text{_____ V} & v_c(0^+) &= \text{_____ V} & v_i(0^+) &= \text{_____ V} \\ v_1(\infty) &= \text{_____ V} & v_2(\infty) &= \text{_____ V} & v_c(\infty) &= \text{_____ V} & v_i(\infty) &= \text{_____ V} \end{aligned}$$

$$\tau = \text{_____ } \mu\text{s}$$
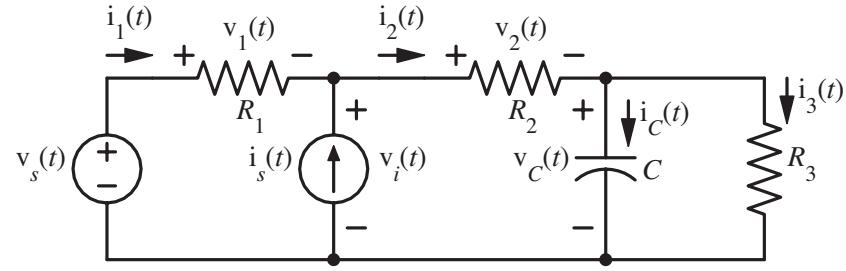
$$\begin{aligned} v_s(t) &= 40 + 20u(t), i_s(t) = 2u(-t), R_1 = 4\Omega \\ R_2 &= 11\Omega, R_3 = 9\Omega, C = 10\mu\text{F} \end{aligned}$$



$$\begin{aligned} i_1(0^-) &= \frac{v_s(0^-)}{R_1 + R_2 + R_3} - i_s(0^-) \frac{R_2 + R_3}{R_1 + R_2 + R_3} = \frac{40}{24} - 2 \frac{20}{24} = 0 \\ v_1(0^-) &= i_1(0^-) R_1 = 0V \end{aligned}$$

$$\begin{aligned} i_2(0^-) &= \frac{v_s(0^-)}{R_1 + R_2 + R_3} + i_s(0^-) \frac{R_1}{R_1 + R_2 + R_3} = \frac{40}{24} + 2 \frac{4}{24} = 2A \\ v_2(0^-) &= i_2(0^-) R_2 = 22V \end{aligned}$$

$$\begin{aligned} i_1(0^-) &= 0A & i_2(0^-) &= 2A & i_3(0^-) &= i_2(0^-) = 2A & i_c(0^-) &= 0A \\ i_1(0^+) &= \frac{v_s(0^+) - v_c(0^+)}{R_1 + R_2} = 42/15 = 2.8A & i_2(0^+) &= i_1(0^+) = 2.8A & i_3(0^+) &= v_c(0^+)/R_3 = 2A & i_c(0^+) &= i_2(0^+) - i_3(0^+) = 0.8A \\ i_1(\infty) &= \frac{v_s(\infty)}{R_1 + R_2 + R_3} = \frac{60}{24} = 2.5A & i_2(\infty) &= i_1(\infty) = 2.5A & i_3(\infty) &= i_1(\infty) = 2.5A & i_c(\infty) &= 0A \end{aligned}$$

$$\begin{aligned} v_1(0^-) &= 0V & v_2(0^-) &= 22V & v_c(0^-) &= i_3(0^-) R_3 = 18V & v_i(0^-) &= v_c(0^-) + v_2(0^-) = 40V \\ v_1(0^+) &= i_1(0^+) R_1 = 11.2V & v_2(0^+) &= i_2(0^+) R_2 = 30.8V & v_c(0^+) &= v_c(0^-) = 18V & v_i(0^+) &= v_c(0^+) + v_2(0^+) = 48.8V \\ v_1(\infty) &= i_1(\infty) R_1 = 10V & v_2(\infty) &= i_2(\infty) R_2 = 27.5V & v_c(\infty) &= i_3(\infty) R_3 = 22.5V & v_i(\infty) &= v_c(\infty) + v_2(\infty) = 50V \end{aligned}$$

$$\tau = R_{eq} C = R_3 \parallel (R_1 + R_2) C = 56.25 \mu\text{s}$$

Solution of ECE 300 Test 7 F11

1. Fill in the blanks with numbers.

$$v_1(0^-) = \text{_____} \text{ V} \quad v_2(0^-) = \text{_____} \text{ V} \quad v_L(0^-) = \text{_____} \text{ V}$$


$$v_1(0^+) = \text{_____} \text{ V} \quad v_2(0^+) = \text{_____} \text{ V} \quad v_L(0^+) = \text{_____} \text{ V}$$

$$i_l(0^-) = \text{_____} \text{ A} \quad i_L(0^-) = \text{_____} \text{ A}$$

$$i_l(0^+) = \text{_____} \text{ A} \quad i_L(0^+) = \text{_____} \text{ A}$$

$$\tau = \text{_____} \text{ ms}$$
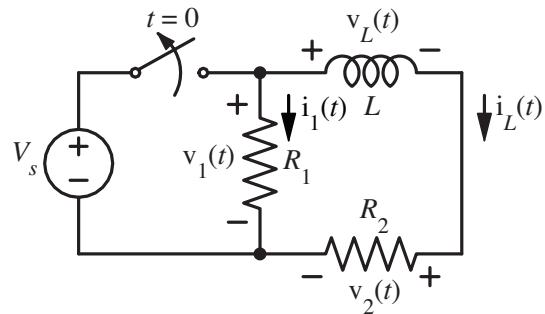
$$V_s = 21 \text{ V}, R_1 = 9 \Omega, R_2 = 20 \Omega, L = 150 \text{ mH}$$



$$v_1(0^-) = V_s = 21 \text{ V} \quad v_2(0^-) = V_s = 21 \text{ V} \quad v_L(0^-) = 0 \text{ V}$$

$$v_1(0^+) = i_l(0^+) \times R_1 = -9.45 \text{ V} \quad v_2(0^+) = i_L(0^+) \times R_2 = 21 \text{ V} \quad v_L(0^+) = v_1(0^+) - v_2(0^+) = -30.45 \text{ V}$$

$$i_l(0^-) = V_s / R_1 = 21 / 9 = 2.333 \text{ A} \quad i_L(0^-) = V_s / R_2 = 21 / 20 = 1.05 \text{ A}$$

$$i_l(0^+) = -i_L(0^+) = -1.05 \text{ A} \quad i_L(0^+) = i_l(0^-) = 1.05 \text{ A}$$

$$\tau = L / R_{eq} = 0.15 / 29 = 5.17 \text{ ms}$$


2. Fill in the blanks with numbers.

$$\begin{aligned} i_1(0^-) &= \text{_____ A} & i_2(0^-) &= \text{_____ A} & i_3(0^-) &= \text{_____ A} & i_c(0^-) &= \text{_____ A} \\ i_1(0^+) &= \text{_____ A} & i_2(0^+) &= \text{_____ A} & i_3(0^+) &= \text{_____ A} & i_c(0^+) &= \text{_____ A} \\ i_1(\infty) &= \text{_____ A} & i_2(\infty) &= \text{_____ A} & i_3(\infty) &= \text{_____ A} & i_c(\infty) &= \text{_____ A} \end{aligned}$$

$$\begin{aligned} v_1(0^-) &= \text{_____ V} & v_2(0^-) &= \text{_____ V} & v_c(0^-) &= \text{_____ V} & v_i(0^-) &= \text{_____ V} \\ v_1(0^+) &= \text{_____ V} & v_2(0^+) &= \text{_____ V} & v_c(0^+) &= \text{_____ V} & v_i(0^+) &= \text{_____ V} \\ v_1(\infty) &= \text{_____ V} & v_2(\infty) &= \text{_____ V} & v_c(\infty) &= \text{_____ V} & v_i(\infty) &= \text{_____ V} \end{aligned}$$

$$\tau = \text{_____ } \mu\text{s}$$
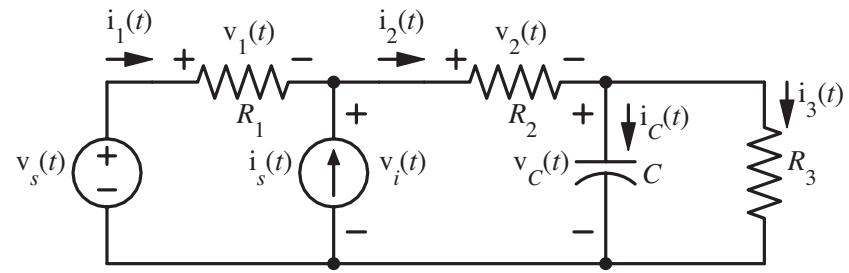
$$\begin{aligned} v_s(t) &= 20 + 10u(t), i_s(t) = u(-t), R_1 = 4\Omega \\ R_2 &= 11\Omega, R_3 = 9\Omega, C = 10\mu\text{F} \end{aligned}$$



$$i_1(0^-) = \frac{v_s(0^-)}{R_1 + R_2 + R_3} - i_s(0^-) \frac{R_2 + R_3}{R_1 + R_2 + R_3} = \frac{20}{24} - \frac{20}{24} = 0$$

$$v_1(0^-) = i_1(0^-)R_1 = 0V$$

$$i_2(0^-) = \frac{v_s(0^-)}{R_1 + R_2 + R_3} + i_s(0^-) \frac{R_1}{R_1 + R_2 + R_3} = \frac{20}{24} + \frac{4}{24} = 1A$$

$$v_2(0^-) = i_2(0^-)R_2 = 11V$$

$$i_1(0^-) = 0A$$

$$i_2(0^-) = 1A$$

$$i_3(0^-) = i_2(0^-) = 1A$$

$$i_c(0^-) = 0A$$

$$i_1(0^+) = \frac{v_s(0^+) - v_c(0^+)}{R_1 + R_2} = 21/15 = 1.4A \quad i_2(0^+) = i_1(0^+) = 1.4A \quad i_3(0^+) = v_c(0^+)/R_3 = 1A \quad i_c(0^+) = i_2(0^+) - i_3(0^+) = 0.4A$$

$$i_1(\infty) = \frac{v_s(\infty)}{R_1 + R_2 + R_3} = \frac{60}{24} = 1.25A \quad i_2(\infty) = i_1(\infty) = 1.25A \quad i_3(\infty) = i_1(\infty) = 1.25A \quad i_c(\infty) = 0A$$

$$\begin{aligned} v_1(0^-) &= 0V & v_2(0^-) &= 11V & v_c(0^-) &= i_3(0^-)R_3 = 9V & v_i(0^-) &= v_c(0^-) + v_2(0^-) = 20V \\ v_1(0^+) &= i_1(0^+)R_1 = 5.6V & v_2(0^+) &= i_2(0^+)R_2 = 15.4V & v_c(0^+) &= v_c(0^-) = 9V & v_i(0^+) &= v_c(0^+) + v_2(0^+) = 24.4V \\ v_1(\infty) &= i_1(\infty)R_1 = 5V & v_2(\infty) &= i_2(\infty)R_2 = 13.75V & v_c(\infty) &= i_3(\infty)R_3 = 11.25V & v_i(\infty) &= v_c(\infty) + v_2(\infty) = 25V \end{aligned}$$

$$\tau = R_{eq}C = R_3 \parallel (R_1 + R_2)C = 56.25 \mu\text{s}$$

Solution of ECE 300 Test 7 F11

1. Fill in the blanks with numbers.

$$v_i(0^-) = \text{_____} V \quad v_2(0^-) = \text{_____} V \quad v_L(0^-) = \text{_____} V$$


$$v_i(0^+) = \text{_____} V \quad v_2(0^+) = \text{_____} V \quad v_L(0^+) = \text{_____} V$$

$$i_i(0^-) = \text{_____} A \quad i_L(0^-) = \text{_____} A$$

$$i_i(0^+) = \text{_____} A \quad i_L(0^+) = \text{_____} A$$

$$\tau = \text{_____} \text{ ms}$$
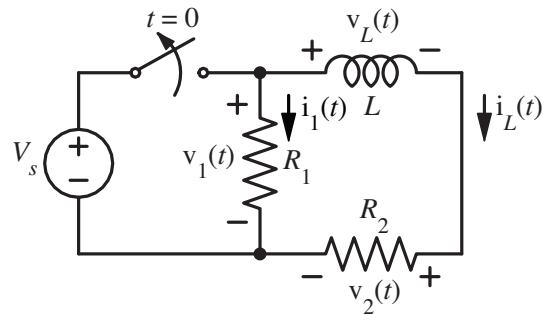
$$V_s = 7V, R_1 = 9\Omega, R_2 = 20\Omega, L = 150 \text{ mH}$$



$$v_i(0^-) = V_s = 7V \quad v_2(0^-) = V_s = 7V \quad v_L(0^-) = 0V$$

$$v_i(0^+) = i_i(0^+) \times R_1 = -3.15V \quad v_2(0^+) = i_L(0^+) \times R_2 = 7V \quad v_L(0^+) = v_i(0^+) - v_2(0^+) = -10.15V$$

$$i_i(0^-) = V_s / R_1 = 7 / 9 = 0.7778 \text{ A} \quad i_L(0^-) = V_s / R_2 = 7 / 20 = 0.35 \text{ A}$$

$$i_i(0^+) = -i_L(0^+) = -0.35 \text{ A} \quad i_L(0^+) = i_L(0^-) = 0.35 \text{ A}$$

$$\tau = L / R_{eq} = 0.15 / 29 = 5.17 \text{ ms}$$


2. Fill in the blanks with numbers.

$$\begin{aligned} i_1(0^-) &= \text{_____ A} & i_2(0^-) &= \text{_____ A} & i_3(0^-) &= \text{_____ A} & i_c(0^-) &= \text{_____ A} \\ i_1(0^+) &= \text{_____ A} & i_2(0^+) &= \text{_____ A} & i_3(0^+) &= \text{_____ A} & i_c(0^+) &= \text{_____ A} \\ i_1(\infty) &= \text{_____ A} & i_2(\infty) &= \text{_____ A} & i_3(\infty) &= \text{_____ A} & i_c(\infty) &= \text{_____ A} \end{aligned}$$

$$\begin{aligned} v_1(0^-) &= \text{_____ V} & v_2(0^-) &= \text{_____ V} & v_c(0^-) &= \text{_____ V} & v_i(0^-) &= \text{_____ V} \\ v_1(0^+) &= \text{_____ V} & v_2(0^+) &= \text{_____ V} & v_c(0^+) &= \text{_____ V} & v_i(0^+) &= \text{_____ V} \\ v_1(\infty) &= \text{_____ V} & v_2(\infty) &= \text{_____ V} & v_c(\infty) &= \text{_____ V} & v_i(\infty) &= \text{_____ V} \end{aligned}$$

$$\tau = \text{_____ } \mu\text{s}$$
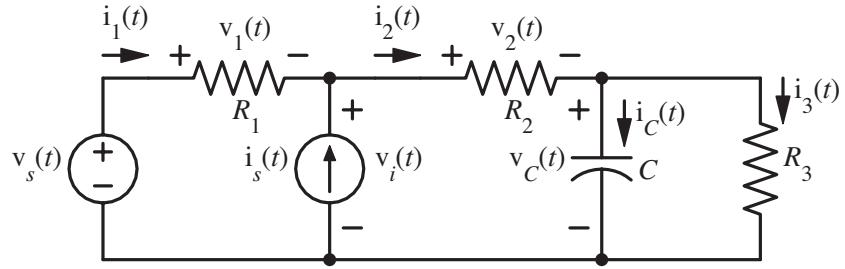
$$\begin{aligned} v_s(t) &= 80 + 40u(t), i_s(t) = 4u(-t), R_l = 4\Omega \\ R_2 &= 11\Omega, R_3 = 9\Omega, C = 10\mu\text{F} \end{aligned}$$



$$\begin{aligned} i_1(0^-) &= \frac{v_s(0^-)}{R_1 + R_2 + R_3} - i_s(0^-) \frac{R_2 + R_3}{R_1 + R_2 + R_3} = \frac{80}{24} - 4 \frac{20}{24} = 0 \\ v_1(0^-) &= i_1(0^-) R_1 = 0V \end{aligned}$$

$$\begin{aligned} i_2(0^-) &= \frac{v_s(0^-)}{R_1 + R_2 + R_3} + i_s(0^-) \frac{R_1}{R_1 + R_2 + R_3} = \frac{80}{24} + 4 \frac{4}{24} = 4A \\ v_2(0^-) &= i_2(0^-) R_2 = 44V \end{aligned}$$

$$\begin{aligned} i_1(0^-) &= 0A & i_2(0^-) &= 4A & i_3(0^-) &= i_2(0^-) = 4A & i_c(0^-) &= 0A \\ i_1(0^+) &= \frac{v_s(0^+) - v_c(0^+)}{R_1 + R_2} = 84/15 = 5.6A & i_2(0^+) &= i_1(0^+) = 5.6A & i_3(0^+) &= v_c(0^+)/R_3 = 4A & i_c(0^+) &= i_2(0^+) - i_3(0^+) = 1.6A \\ i_1(\infty) &= \frac{v_s(\infty)}{R_1 + R_2 + R_3} = \frac{60}{24} = 5A & i_2(\infty) &= i_1(\infty) = 5A & i_3(\infty) &= i_1(\infty) = 5A & i_c(\infty) &= 0A \end{aligned}$$

$$\begin{aligned} v_1(0^-) &= 0V & v_2(0^-) &= 44V & v_c(0^-) &= i_3(0^-) R_3 = 36V & v_i(0^-) &= v_c(0^-) + v_2(0^-) = 80V \\ v_1(0^+) &= i_1(0^+) R_1 = 22.4V & v_2(0^+) &= i_2(0^+) R_2 = 61.6V & v_c(0^+) &= v_c(0^-) = 36V & v_i(0^+) &= v_c(0^+) + v_2(0^+) = 97.6V \\ v_1(\infty) &= i_1(\infty) R_1 = 20V & v_2(\infty) &= i_2(\infty) R_2 = 55V & v_c(\infty) &= i_3(\infty) R_3 = 45V & v_i(\infty) &= v_c(\infty) + v_2(\infty) = 100V \end{aligned}$$

$$\tau = R_{eq} C = R_3 \parallel (R_1 + R_2) C = 56.25 \mu\text{s}$$