


Solution of ECE 300 Test 7 S12

1. Fill in the blanks with correct numbers.

$$\begin{aligned}
 i_1(0^-) &= \text{_____ mA} & i_2(0^-) &= \text{_____ mA} & i_c(0^-) &= \text{_____ mA} \\
 v_1(0^-) &= \text{_____ V} & v_c(0^-) &= \text{_____ V} & v_3(0^-) &= \text{_____ V} \\
 i_1(0^+) &= \text{_____ mA} & i_2(0^+) &= \text{_____ mA} & i_c(0^+) &= \text{_____ mA} \\
 v_1(0^+) &= \text{_____ V} & v_c(0^+) &= \text{_____ V} & v_3(0^+) &= \text{_____ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is _____ ms
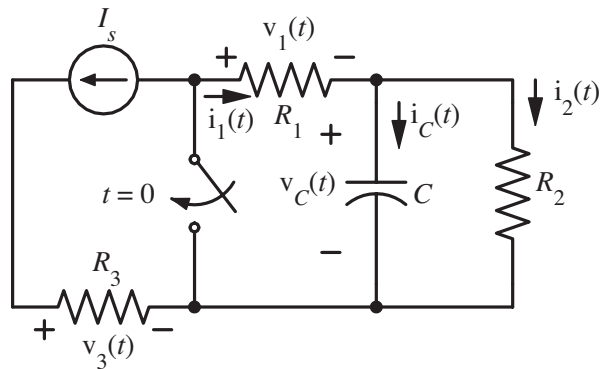
$$\begin{aligned}
 I_s &= 2 \text{ mA}, R_1 = 2.3 \text{ k}\Omega, R_2 = 1.8 \text{ k}\Omega \\
 R_3 &= 900 \Omega, C = 22 \mu\text{F}
 \end{aligned}$$



At $t = 0^-$, the switch is open, the capacitor is equivalent to an open circuit and all the I_s current flows through the three resistors counterclockwise. The voltage across the capacitor is $i_2 R_2 = -I_s R_2$ and does not change instantaneously when the switch is closed. So at $t = 0^+$ the switch is closed and the capacitor voltage and the current i_2 stay the same. The resistor R_1 is now in parallel with the capacitor so $v_1 = -v_c$ and $i_1 = v_1 / R_1$. The voltage across R_3 stays the same because it is in series with a current source that is constant. The time constant is $\tau = R_{eq} C$ where $R_{eq} = R_1 \parallel R_2$.

$$\begin{aligned}
 i_1(0^-) &= -2 \text{ mA} & i_2(0^-) &= -2 \text{ mA} & i_c(0^-) &= 0 \text{ mA} \\
 v_1(0^-) &= -4.6 \text{ V} & v_c(0^-) &= -3.6 \text{ V} & v_3(0^-) &= 1.8 \text{ V} \\
 i_1(0^+) &= 1.5652 \text{ mA} & i_2(0^+) &= -2 \text{ mA} & i_c(0^+) &= 3.5652 \text{ mA} \\
 v_1(0^+) &= 3.6 \text{ V} & v_c(0^+) &= -3.6 \text{ V} & v_3(0^+) &= 1.8 \text{ V}
 \end{aligned}$$


For $t > 0$, the time constant τ is 22.2 ms.

2. Fill in the blanks with correct numbers.

$$\begin{aligned}
 i_1(0^-) &= \text{_____ mA} & i_2(0^-) &= \text{_____ mA} & i_L(0^-) &= \text{_____ mA} \\
 v_1(0^-) &= \text{_____ V} & v_L(0^-) &= \text{_____ V} & v_{ds}(0^-) &= \text{_____ V} \\
 i_1(0^+) &= \text{_____ mA} & i_2(0^+) &= \text{_____ mA} & i_L(0^+) &= \text{_____ mA} \\
 v_1(0^+) &= \text{_____ V} & v_L(0^+) &= \text{_____ V} & v_{ds}(0^+) &= \text{_____ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is _____ μs .
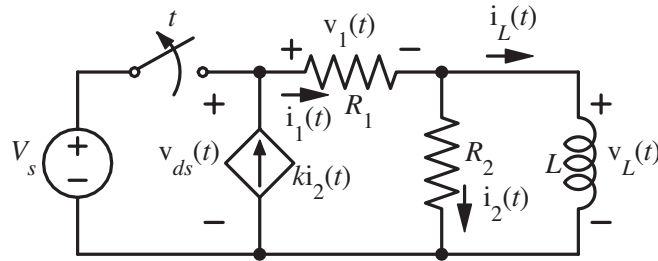
$$\begin{aligned}
 V_s &= 12 \text{ V}, R_1 = 5.3 \text{ k}\Omega, R_2 = 8.8 \text{ k}\Omega \\
 L &= 24 \text{ mH}, k = 0.6
 \end{aligned}$$



At $t = 0^-$, the switch is closed, the inductor is equivalent to a short circuit so the voltage across it is zero, making the voltage across R_2 zero, making the current i_2 zero, making the current ki_2 also zero. So $v_1 = V_s$ and the current through both R_1 and the inductor is V_s / R_1 . At $t = 0^+$, $i_L + i_2 = ki_2$ (because the switch is now open) therefore $i_2 = \frac{i_L}{k-1}$. The currents ki_2 and i_1 are the same and $v_1 = i_1 R_1$. Also $v_L = i_2 R_2$ and $v_{ds} = v_L + v_1$. For $t > 0$, the equivalent resistance in parallel with the inductor is the Thevenin equivalent resistance of the network formed by the two resistors and the dependent source. Applying a 1 V test source at the load terminals of that network the current i_s flowing into the network is set by $i_2 = ki_2 + i_s$ and $i_2 = 1 / R_2$. Solving, $i_s = (1 - k) / R_2$ and $R_{eq} = R_2 / (1 - k)$ and $\tau = L / R_{eq} = (1 - k)L / R_2$.

$$\begin{aligned}
 i_1(0^-) &= 2.2642 \text{ mA} & i_2(0^-) &= 0 \text{ mA} & i_L(0^-) &= 2.2642 \text{ mA} \\
 v_1(0^-) &= 12 \text{ V} & v_L(0^-) &= 0 \text{ V} & v_{ds}(0^-) &= 12 \text{ V} \\
 i_1(0^+) &= -3.3962 \text{ mA} & i_2(0^+) &= -5.6604 \text{ mA} & i_L(0^+) &= 2.2642 \text{ mA} \\
 v_1(0^+) &= -18 \text{ V} & v_L(0^+) &= -49.8115 \text{ V} & v_{ds}(0^+) &= -67.8115 \text{ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is 1.091 μs .


Solution of ECE 300 Test 7 S12

1. Fill in the blanks with correct numbers.

$$\begin{aligned}
 i_1(0^-) &= \text{_____ mA} & i_2(0^-) &= \text{_____ mA} & i_c(0^-) &= \text{_____ mA} \\
 v_1(0^-) &= \text{_____ V} & v_c(0^-) &= \text{_____ V} & v_3(0^-) &= \text{_____ V} \\
 i_1(0^+) &= \text{_____ mA} & i_2(0^+) &= \text{_____ mA} & i_c(0^+) &= \text{_____ mA} \\
 v_1(0^+) &= \text{_____ V} & v_c(0^+) &= \text{_____ V} & v_3(0^+) &= \text{_____ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is _____ ms
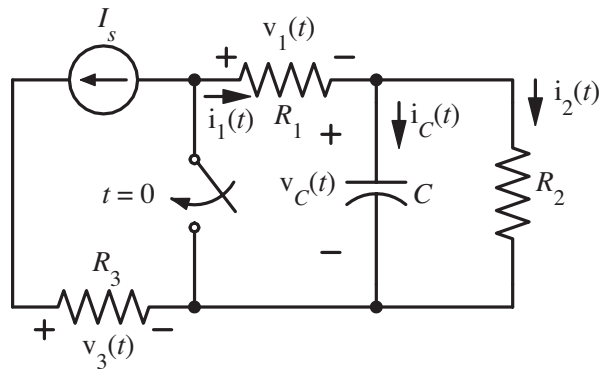
$$\begin{aligned}
 I_s &= 1 \text{ mA}, R_1 = 2.3 \text{ k}\Omega, R_2 = 1.8 \text{ k}\Omega \\
 R_3 &= 900 \Omega, C = 47 \mu\text{F}
 \end{aligned}$$



At $t = 0^-$, the switch is open, the capacitor is equivalent to an open circuit and all the I_s current flows through the three resistors counterclockwise. The voltage across the capacitor is $i_2 R_2 = -I_s R_2$ and does not change instantaneously when the switch is closed. So at $t = 0^+$ the switch is closed and the capacitor voltage and the current i_2 stay the same. The resistor R_1 is now in parallel with the capacitor so $v_1 = -v_c$ and $i_1 = v_1 / R_1$. The voltage across R_3 stays the same because it is in series with a current source that is constant. The time constant is $\tau = R_{eq} C$ where $R_{eq} = R_1 \parallel R_2$.

$$\begin{aligned}
 i_1(0^-) &= -1 \text{ mA} & i_2(0^-) &= -1 \text{ mA} & i_c(0^-) &= 0 \text{ mA} \\
 v_1(0^-) &= -2.3 \text{ V} & v_c(0^-) &= -1.8 \text{ V} & v_3(0^-) &= 0.9 \text{ V} \\
 i_1(0^+) &= 0.7826 \text{ mA} & i_2(0^+) &= -1 \text{ mA} & i_c(0^+) &= 1.7826 \text{ mA} \\
 v_1(0^+) &= 1.8 \text{ V} & v_c(0^+) &= -1.8 \text{ V} & v_3(0^+) &= 0.9 \text{ V}
 \end{aligned}$$


For $t > 0$, the time constant τ is 47.43 ms.

2. Fill in the blanks with correct numbers.

$$\begin{aligned}
 i_1(0^-) &= \text{_____ mA} & i_2(0^-) &= \text{_____ mA} & i_L(0^-) &= \text{_____ mA} \\
 v_1(0^-) &= \text{_____ V} & v_L(0^-) &= \text{_____ V} & v_{ds}(0^-) &= \text{_____ V} \\
 i_1(0^+) &= \text{_____ mA} & i_2(0^+) &= \text{_____ mA} & i_L(0^+) &= \text{_____ mA} \\
 v_1(0^+) &= \text{_____ V} & v_L(0^+) &= \text{_____ V} & v_{ds}(0^+) &= \text{_____ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is _____ μs .
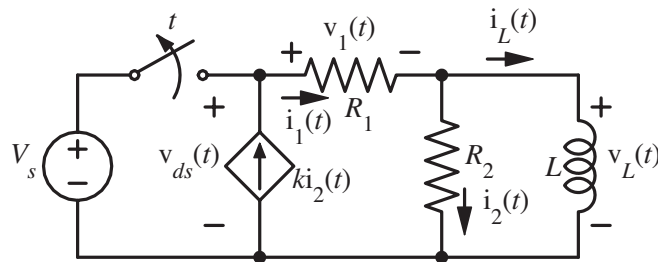
$$\begin{aligned}
 V_s &= 24 \text{ V}, R_1 = 5.3 \text{ k}\Omega, R_2 = 8.8 \text{ k}\Omega \\
 L &= 12 \text{ mH}, k = 0.6
 \end{aligned}$$



At $t = 0^-$, the switch is closed, the inductor is equivalent to a short circuit so the voltage across it is zero, making the voltage across R_2 zero, making the current i_2 zero, making the current ki_2 also zero. So $v_1 = V_s$ and the current through both R_1 and the inductor is V_s / R_1 . At $t = 0^+$, $i_L + i_2 = ki_2$ (because the switch is now open) therefore $i_2 = \frac{i_L}{k-1}$. The currents ki_2 and i_1 are the same and $v_1 = i_1 R_1$. Also $v_L = i_2 R_2$ and $v_{ds} = v_L + v_1$. For $t > 0$, the equivalent resistance in parallel with the inductor is the Thevenin equivalent resistance of the network formed by the two resistors and the dependent source. Applying a 1 V test source at the load terminals of that network the current i_s flowing into the network is set by $i_2 = ki_2 + i_s$ and $i_2 = 1 / R_2$. Solving, $i_s = (1-k) / R_2$ and $R_{eq} = R_2 / (1-k)$ and $\tau = L / R_{eq} = (1-k)L / R_2$.

$$\begin{aligned}
 i_1(0^-) &= 4.5284 \text{ mA} & i_2(0^-) &= 0 \text{ mA} & i_L(0^-) &= 4.5284 \text{ mA} \\
 v_1(0^-) &= 24 \text{ V} & v_L(0^-) &= 0 \text{ V} & v_{ds}(0^-) &= 24 \text{ V} \\
 i_1(0^+) &= -6.7924 \text{ mA} & i_2(0^+) &= -11.3208 \text{ mA} & i_L(0^+) &= 4.5284 \text{ mA} \\
 v_1(0^+) &= -36 \text{ V} & v_L(0^+) &= -99.623 \text{ V} & v_{ds}(0^+) &= -135.623 \text{ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is 0.5455 μs .


Solution of ECE 300 Test 7 S12

1. Fill in the blanks with correct numbers.

$$\begin{aligned}
 i_1(0^-) &= \text{_____ mA} & i_2(0^-) &= \text{_____ mA} & i_c(0^-) &= \text{_____ mA} \\
 v_1(0^-) &= \text{_____ V} & v_c(0^-) &= \text{_____ V} & v_3(0^-) &= \text{_____ V} \\
 i_1(0^+) &= \text{_____ mA} & i_2(0^+) &= \text{_____ mA} & i_c(0^+) &= \text{_____ mA} \\
 v_1(0^+) &= \text{_____ V} & v_c(0^+) &= \text{_____ V} & v_3(0^+) &= \text{_____ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is _____ ms
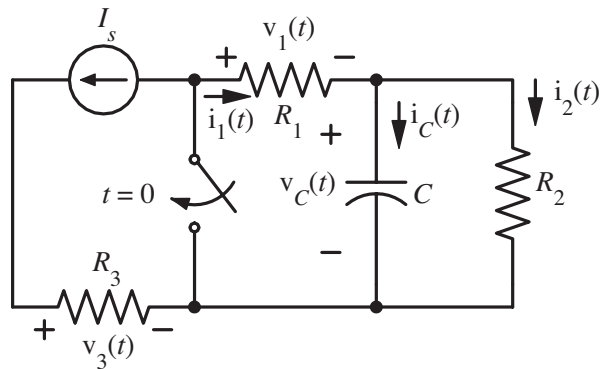
$$\begin{aligned}
 I_s &= 4 \text{ mA}, R_1 = 2.3 \text{ k}\Omega, R_2 = 1.8 \text{ k}\Omega \\
 R_3 &= 900 \Omega, C = 44 \mu\text{F}
 \end{aligned}$$



At $t = 0^-$, the switch is open, the capacitor is equivalent to an open circuit and all the I_s current flows through the three resistors counterclockwise. The voltage across the capacitor is $i_2 R_2 = -I_s R_2$ and does not change instantaneously when the switch is closed. So at $t = 0^+$ the switch is closed and the capacitor voltage and the current i_2 stay the same. The resistor R_1 is now in parallel with the capacitor so $v_1 = -v_c$ and $i_1 = v_1 / R_1$. The voltage across R_3 stays the same because it is in series with a current source that is constant. The time constant is $\tau = R_{eq} C$ where $R_{eq} = R_1 \parallel R_2$.

$$\begin{aligned}
 i_1(0^-) &= -4 \text{ mA} & i_2(0^-) &= -4 \text{ mA} & i_c(0^-) &= 0 \text{ mA} \\
 v_1(0^-) &= -9.2 \text{ V} & v_c(0^-) &= -7.2 \text{ V} & v_3(0^-) &= 3.6 \text{ V} \\
 i_1(0^+) &= 3.1304 \text{ mA} & i_2(0^+) &= -4 \text{ mA} & i_c(0^+) &= 7.1304 \text{ mA} \\
 v_1(0^+) &= 7.2 \text{ V} & v_c(0^+) &= -7.2 \text{ V} & v_3(0^+) &= 3.6 \text{ V}
 \end{aligned}$$


For $t > 0$, the time constant τ is 44.4 ms.

2. Fill in the blanks with correct numbers.

$$\begin{aligned}
 i_1(0^-) &= \text{_____ mA} & i_2(0^-) &= \text{_____ mA} & i_L(0^-) &= \text{_____ mA} \\
 v_1(0^-) &= \text{_____ V} & v_L(0^-) &= \text{_____ V} & v_{ds}(0^-) &= \text{_____ V} \\
 i_1(0^+) &= \text{_____ mA} & i_2(0^+) &= \text{_____ mA} & i_L(0^+) &= \text{_____ mA} \\
 v_1(0^+) &= \text{_____ V} & v_L(0^+) &= \text{_____ V} & v_{ds}(0^+) &= \text{_____ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is _____ μs .
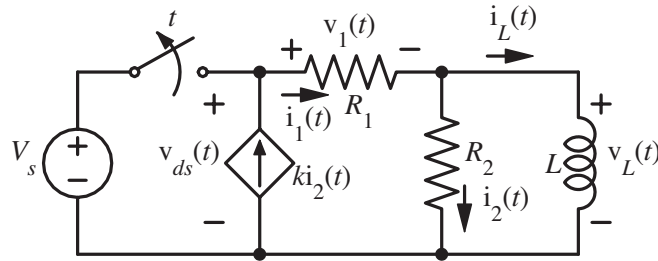
$$\begin{aligned}
 V_s &= 6 \text{ V}, R_1 = 5.3 \text{ k}\Omega, R_2 = 8.8 \text{ k}\Omega \\
 L &= 48 \text{ mH}, k = 0.6
 \end{aligned}$$



At $t = 0^-$, the switch is closed, the inductor is equivalent to a short circuit so the voltage across it is zero, making the voltage across R_2 zero, making the current i_2 zero, making the current ki_2 also zero. So $v_1 = V_s$ and the current through both R_1 and the inductor is V_s / R_1 . At $t = 0^+$, $i_L + i_2 = ki_2$ (because the switch is now open) therefore $i_2 = \frac{i_L}{k-1}$. The currents ki_2 and i_1 are the same and $v_1 = i_1 R_1$. Also $v_L = i_2 R_2$ and $v_{ds} = v_L + v_1$. For $t > 0$, the equivalent resistance in parallel with the inductor is the Thevenin equivalent resistance of the network formed by the two resistors and the dependent source. Applying a 1 V test source at the load terminals of that network the current i_s flowing into the network is set by $i_2 = ki_2 + i_s$ and $i_2 = 1 / R_2$. Solving, $i_s = (1-k) / R_2$ and $R_{eq} = R_2 / (1-k)$ and $\tau = L / R_{eq} = (1-k)L / R_2$.

$$\begin{aligned}
 i_1(0^-) &= 1.1321 \text{ mA} & i_2(0^-) &= 0 \text{ mA} & i_L(0^-) &= 1.1321 \text{ mA} \\
 v_1(0^-) &= 6 \text{ V} & v_L(0^-) &= 0 \text{ V} & v_{ds}(0^-) &= 6 \text{ V} \\
 i_1(0^+) &= -1.6981 \text{ mA} & i_2(0^+) &= -2.8302 \text{ mA} & i_L(0^+) &= 1.1321 \text{ mA} \\
 v_1(0^+) &= -9 \text{ V} & v_L(0^+) &= -24.4058 \text{ V} & v_{ds}(0^+) &= -33.9057 \text{ V}
 \end{aligned}$$

For $t > 0$, the time constant τ is 2.182 μs .