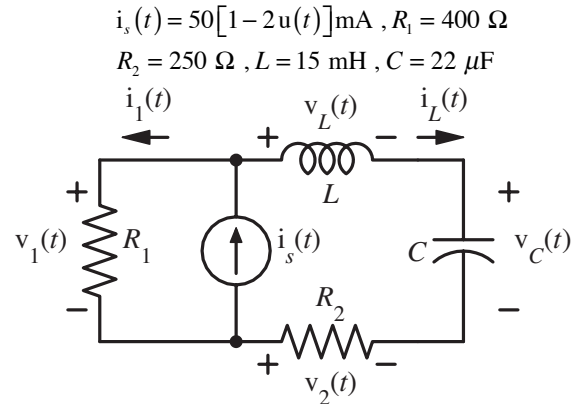


Solution of ECE 300 Test 9 F10

1. (a) Fill in the table below with numbers.



$$\begin{array}{llll}
 v_1(0^-) = 20\ \text{V} & v_2(0^-) = 0\ \text{V} & v_L(0^-) = 0\ \text{V} & v_C(0^-) = 20\ \text{V} \\
 v_1(0^+) = -20\ \text{V} & v_2(0^+) = 0\ \text{V} & v_L(0^+) = -40\ \text{V} & v_C(0^+) = 20\ \text{V} \\
 v_1(\infty) = -20\ \text{V} & v_2(\infty) = 0\ \text{V} & v_L(\infty) = 0\ \text{V} & v_C(\infty) = -20\ \text{V}
 \end{array}$$

$$\begin{array}{ll}
 i_1(0^-) = 50\ \text{mA} & i_L(0^-) = 0\ \text{mA} \\
 i_1(0^+) = -50\ \text{mA} & i_L(0^+) = 0\ \text{mA} \\
 i_1(\infty) = -50\ \text{mA} & i_L(\infty) = 0\ \text{mA}
 \end{array}$$

- (b) Find these numerical values.

$$\begin{aligned}\alpha &= R / 2L = 650\Omega / 30\text{mH} = 21,667 \\ \omega_0 &= 1 / \sqrt{LC} = 1 / \sqrt{15\text{mH} \times 22\mu\text{F}} = 1740.8 \\ s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -70.04 \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -43,263\end{aligned}$$

- (c) If $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ find the numerical values of A_1 and A_2 .

$$\begin{aligned}v_C(0^+) &= A_1 + A_2 - 20 = 20 \text{ V} \\ \left. \frac{dv_C(t)}{dt} \right|_{t=0^+} &= s_1 A_1 + s_2 A_2 = \frac{i_C(0^+)}{C} = \frac{i_L(0^+)}{C} = 0\end{aligned}$$


$$\begin{bmatrix} 1 & 1 \\ -70.04 & -43263 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 40 \\ 0 \end{bmatrix} \Rightarrow A_1 = 40.0649, A_2 = -0.0649$$

- (d) Find the numerical value of $v_C(0.5 \text{ ms})$.

$$\begin{aligned}v_C(t) &= 40.0649 e^{-70.04t} - 0.0649 e^{-43263t} - 20 \\ v_C(0.5 \text{ ms}) &= 40.0649 e^{-70.04 \times 0.0005} - 0.0649 e^{-43263 \times 0.0005} - 20 = 18.6861 \text{ V}\end{aligned}$$

Solution of ECE 300 Test 9 F10

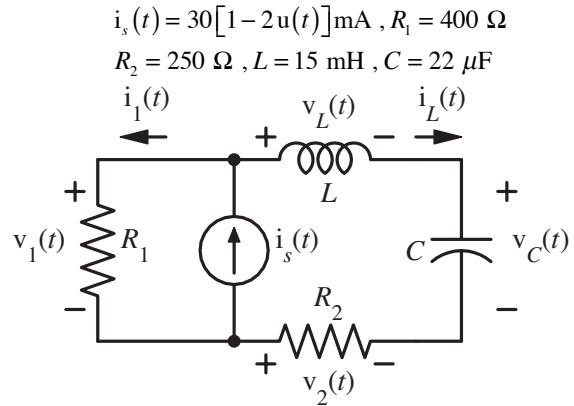1. (a) Fill in the table below with numbers.



| | | | |
|-------------------------------|-----------------------------|-----------------------------|-------------------------------|
| $v_1(0^-) = 12\ \text{V}$ | $v_2(0^-) = 0\ \text{V}$ | $v_L(0^-) = 0\ \text{V}$ | $v_C(0^-) = 12\ \text{V}$ |
| $v_1(0^+) = -12\ \text{V}$ | $v_2(0^+) = 0\ \text{V}$ | $v_L(0^+) = -24\ \text{V}$ | $v_C(0^+) = 12\ \text{V}$ |
| $v_1(\infty) = -12\ \text{V}$ | $v_2(\infty) = 0\ \text{V}$ | $v_L(\infty) = 0\ \text{V}$ | $v_C(\infty) = -12\ \text{V}$ |

| | |
|--------------------------------|------------------------------|
| $i_1(0^-) = 30\ \text{mA}$ | $i_L(0^-) = 0\ \text{mA}$ |
| $i_1(0^+) = -30\ \text{mA}$ | $i_L(0^+) = 0\ \text{mA}$ |
| $i_1(\infty) = -30\ \text{mA}$ | $i_L(\infty) = 0\ \text{mA}$ |

- (b) Find these numerical values.

$$\alpha = R / 2L = 650\Omega / 30\text{mH} = 21,667$$

$$\omega_0 = 1 / \sqrt{LC} = 1 / \sqrt{15\text{mH} \times 22\mu\text{F}} = 1740.8$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -70.04$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -43,263$$

- (c) If $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ find the numerical values of A_1 and A_2 .

$$v_C(0^+) = A_1 + A_2 - 12 = 12 \text{ V}$$

$$\left. \frac{dv_C(t)}{dt} \right|_{t=0^+} = s_1 A_1 + s_2 A_2 = \frac{i_C(0^+)}{C} = \frac{i_L(0^+)}{C} = 0$$

$$\begin{bmatrix} 1 & 1 \\ -70.04 & -43263 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 24 \\ 0 \end{bmatrix} \Rightarrow A_1 = 24.0389, A_2 = -0.0389$$


- (d) Find the numerical value of $v_C(0.5 \text{ ms})$.

$$v_C(t) = 24.0389 e^{-70.04t} - 0.0389 e^{-43263t} - 12$$

$$v_C(0.5 \text{ ms}) = 24.0389 e^{-70.04 \times 0.0005} - 0.0389 e^{-43263 \times 0.0005} - 12 = 11.2116 \text{ V}$$

Solution of ECE 300 Test 9 F10

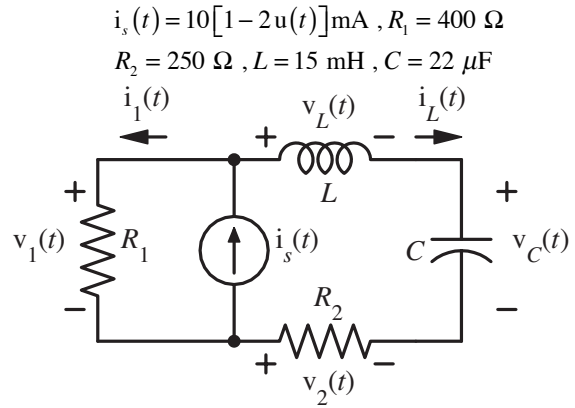1. (a) Fill in the table below with numbers.



| | | | |
|------------------------------|-----------------------------|-----------------------------|------------------------------|
| $v_1(0^-) = 4\ \text{V}$ | $v_2(0^-) = 0\ \text{V}$ | $v_L(0^-) = 0\ \text{V}$ | $v_C(0^-) = 4\ \text{V}$ |
| $v_1(0^+) = -4\ \text{V}$ | $v_2(0^+) = 0\ \text{V}$ | $v_L(0^+) = -8\ \text{V}$ | $v_C(0^+) = 4\ \text{V}$ |
| $v_1(\infty) = -4\ \text{V}$ | $v_2(\infty) = 0\ \text{V}$ | $v_L(\infty) = 0\ \text{V}$ | $v_C(\infty) = -4\ \text{V}$ |

| | |
|--------------------------------|------------------------------|
| $i_1(0^-) = 10\ \text{mA}$ | $i_L(0^-) = 0\ \text{mA}$ |
| $i_1(0^+) = -10\ \text{mA}$ | $i_L(0^+) = 0\ \text{mA}$ |
| $i_1(\infty) = -10\ \text{mA}$ | $i_L(\infty) = 0\ \text{mA}$ |

- (b) Find these numerical values.

$$\alpha = R / 2L = 650\Omega / 30\text{mH} = 21,667$$

$$\omega_0 = 1 / \sqrt{LC} = 1 / \sqrt{15\text{mH} \times 22\mu\text{F}} = 1740.8$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -70.04$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -43,263$$

- (c) If $v_C(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + v_C(\infty)$ find the numerical values of A_1 and A_2 .

$$v_C(0^+) = A_1 + A_2 - 4 = 4 \text{ V}$$

$$\left. \frac{dv_C(t)}{dt} \right|_{t=0^+} = s_1 A_1 + s_2 A_2 = \frac{i_C(0^+)}{C} = \frac{i_L(0^+)}{C} = 0$$

$$\begin{bmatrix} 1 & 1 \\ -70.04 & -43263 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 8 \\ 0 \end{bmatrix} \Rightarrow A_1 = 8.013, A_2 = -0.013$$

- (d) Find the numerical value of $v_C(0.5 \text{ ms})$.

$$v_C(t) = 8.013e^{-70.04t} - 0.013e^{-43263t} - 4$$

$$v_C(0.5 \text{ ms}) = 8.013e^{-70.04 \times 0.0005} - 0.013e^{-43263 \times 0.0005} - 4 = 3.737 \text{ V}$$