

Solution of ECE 300 Test 9 S12


1. Referring to the series *RLC* circuit below,

- (a) Find the numerical values of α and ω_0 . $\alpha = \text{_____ s}^{-1}$, $\omega_0 = \text{_____ s}^{-1}$
- (b) Find the numerical value of $v_L(0^+)$. $v_L(0^+) = \text{_____ V}$
- (c) Find the numerical value of $\frac{d}{dt}(i(t))\Big|_{t=0^+}$. $\frac{d}{dt}(i(t))\Big|_{t=0^+} = \text{_____ A/s}$
- (d) In the solution $v_L(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)] + v_{L_f}$ find the numerical values of B_1 and v_{L_f} .

$$B_1 = \text{_____ V}, v_{L_f} = \text{_____ V}$$

$$v_s(t) = 10 u(t), R = 250 \Omega$$
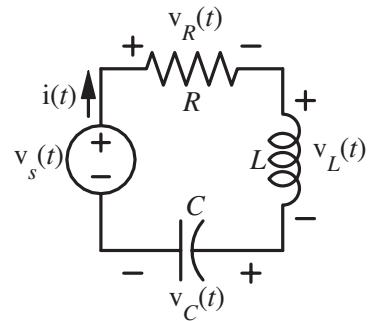
$$L = 30 \text{ mH}, C = 250 \text{ nF}$$



$$\alpha = 4166.7, \omega_0 = 11547, v_L(0^+) = 10, \frac{d}{dt}(i(t))\Big|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{10}{0.03} = 333.333 \text{ A/s}$$

$$B_1 = v_L(0^+) = 10 \text{ V}, v_{L_f} = 0 \text{ V}$$

2. Referring to the parallel RLC circuit below,

(a) Find the numerical values of α and ω_0 . $\alpha = \text{_____ s}^{-1}$, $\omega_0 = \text{_____ s}^{-1}$

(b) Find the numerical value of $i_C(0^+)$. $i_C(0^+) = \text{_____ A}$

(c) Find the numerical value of $\frac{d}{dt}(i_L(t))\Big|_{t=0^+}$. $\frac{d}{dt}(i_L(t))\Big|_{t=0^+} = \text{_____ V/s}$

(d) In the solution $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_{Lf}$ find the numerical values of s_1 , s_2 , A_1 and A_2 and i_{Lf} .

$$s_1 = \text{_____ s}^{-1}, s_2 = \text{_____ s}^{-1}$$


$$A_1 = \text{_____ A}, A_2 = \text{_____ A}, i_{Lf} = \text{_____ A}$$

$$\alpha = 250, \omega_0 = 223.607, i_C(0^+) = -3 \text{ A}, \frac{d}{dt}(i_L(t))\Big|_{t=0^+} = \frac{v(0^+)}{L} = \frac{0 \text{ V}}{0.5 \text{ H}} = 0 \text{ A/s}$$

$$s_1 = -138.197, s_2 = -361.803, A_1 + A_2 = 3, s_1 A_1 + s_2 A_2 = 0$$

$$\begin{bmatrix} 1 & 1 \\ -138.197 & -361.803 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 3 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 4.8541 \\ -1.854 \end{bmatrix}, i_{Lf} = 0 \text{ A}$$
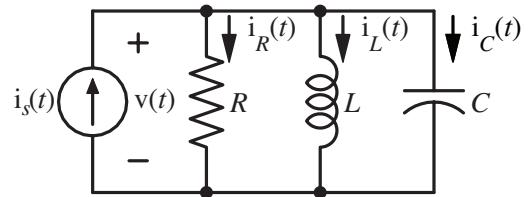
$$i_s(t) = 3u(-t), R = 50\Omega, L = 500 \text{ mH}, C = 40 \mu\text{F}$$



Solution of ECE 300 Test 9 S12


1. Referring to the series *RLC* circuit below,

- (a) Find the numerical values of α and ω_0 . $\alpha = \text{_____ s}^{-1}$, $\omega_0 = \text{_____ s}^{-1}$
- (b) Find the numerical value of $v_L(0^+)$. $v_L(0^+) = \text{_____ V}$
- (c) Find the numerical value of $\frac{d}{dt}(i(t))\Big|_{t=0^+}$. $\frac{d}{dt}(i(t))\Big|_{t=0^+} = \text{_____ A/s}$
- (d) In the solution $v_L(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)] + v_{Lf}$ find the numerical values of B_1 and v_{Lf} .

$$B_1 = \text{_____ V}, v_{Lf} = \text{_____ V}$$

$$v_s(t) = 8 u(t), R = 200\Omega$$
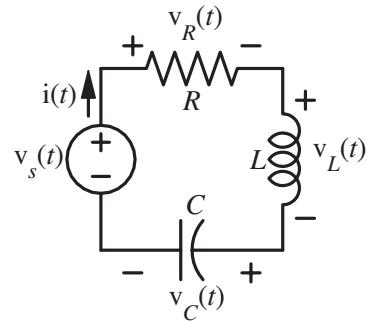
$$L = 35 \text{ mH}, C = 350 \text{ nF}$$



$$\alpha = 2857.1, \omega_0 = 9035.1, v_L(0^+) = 8, \frac{d}{dt}(i(t))\Big|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{8}{0.035} = 228.57 \text{ A/s}$$

$$B_1 = v_L(0^+) = 8 \text{ V}, v_{Lf} = 0 \text{ V}$$

2. Referring to the parallel RLC circuit below,

(a) Find the numerical values of α and ω_0 . $\alpha = \text{_____ s}^{-1}$, $\omega_0 = \text{_____ s}^{-1}$

(b) Find the numerical value of $i_C(0^+)$. $i_C(0^+) = \text{_____ A}$

(c) Find the numerical value of $\frac{d}{dt}(i_L(t))\Big|_{t=0^+}$. $\frac{d}{dt}(i_L(t))\Big|_{t=0^+} = \text{_____ V/s}$

(d) In the solution $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_{Lf}$ find the numerical values of s_1 , s_2 , A_1 and A_2 and i_{Lf} .

$$s_1 = \text{_____ s}^{-1}, s_2 = \text{_____ s}^{-1}$$


$$A_1 = \text{_____ A}, A_2 = \text{_____ A}, i_{Lf} = \text{_____ A}$$

$$\alpha = 416.67, \omega_0 = 258.199, i_C(0^+) = -2 \text{ A}, \frac{d}{dt}(i_L(t))\Big|_{t=0^+} = \frac{v(0^+)}{L} = \frac{0 \text{ V}}{0.5 \text{ H}} = 0 \text{ A/s}$$

$$s_1 = -89.643, s_2 = -743.69, A_1 + A_2 = 2, s_1 A_1 + s_2 A_2 = 0$$

$$\begin{bmatrix} 1 & 1 \\ -89.643 & -743.69 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 2.274 \\ -0.274 \end{bmatrix}, i_{Lf} = 0 \text{ A}$$
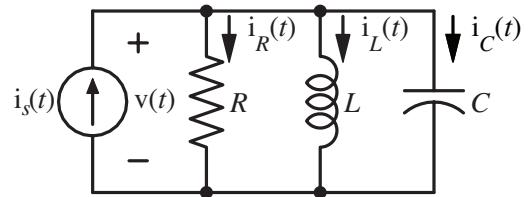
$$i_s(t) = 2 u(-t), R = 40 \Omega, L = 500 \text{ mH}, C = 30 \mu\text{F}$$



Solution of ECE 300 Test 9 S12

1. Referring to the series *RLC* circuit below,

(a) Find the numerical values of α and ω_0 . $\alpha = \text{_____ s}^{-1}$, $\omega_0 = \text{_____ s}^{-1}$

(b) Find the numerical value of $v_L(0^+)$. $v_L(0^+) = \text{_____ V}$


(c) Find the numerical value of $\frac{d}{dt}(i(t))\Big|_{t=0^+}$. $\frac{d}{dt}(i(t))\Big|_{t=0^+} = \text{_____ A/s}$

(d) In the solution $v_L(t) = e^{-\alpha t} [B_1 \cos(\omega_d t) + B_2 \sin(\omega_d t)] + v_{Lf}$ find the numerical values of B_1 and v_{Lf} .

$$B_1 = \text{_____ V}, v_{Lf} = \text{_____ V}$$

$$v_s(t) = 5u(t), R = 150\Omega$$

$$L = 40\text{mH}, C = 450\text{nF}$$

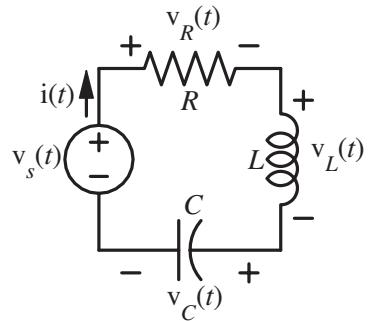

$$\alpha = 1875, \omega_0 = 7453.6, v_L(0^+) = 5, \frac{d}{dt}(i(t))\Big|_{t=0^+} = \frac{v_L(0^+)}{L} = \frac{5}{0.04} = 125 \text{ A/s}$$

$$B_1 = v_L(0^+) = 5V, v_{Lf} = 0V$$

2. Referring to the parallel RLC circuit below,

(a) Find the numerical values of α and ω_0 . $\alpha = \text{_____ s}^{-1}$, $\omega_0 = \text{_____ s}^{-1}$

(b) Find the numerical value of $i_C(0^+)$. $i_C(0^+) = \text{_____ A}$

(c) Find the numerical value of $\frac{d}{dt}(i_L(t))\Big|_{t=0^+}$. $\frac{d}{dt}(i_L(t))\Big|_{t=0^+} = \text{_____ V/s}$

(d) In the solution $i_L(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t} + i_{Lf}$ find the numerical values of s_1 , s_2 , A_1 and A_2 and i_{Lf} .

$$s_1 = \text{_____ s}^{-1}, s_2 = \text{_____ s}^{-1}$$

$$A_1 = \text{_____ A}, A_2 = \text{_____ A}, i_{Lf} = \text{_____ A}$$

$$\alpha = 200, \omega_0 = 141.42, i_C(0^+) = -4 \text{ A}, \frac{d}{dt}(i_L(t))\Big|_{t=0^+} = \frac{v(0^+)}{L} = \frac{0}{0.5 \text{ H}} = 0 \text{ A/s}$$

$$s_1 = -58.579, s_2 = -341.421, A_1 + A_2 = 4, s_1 A_1 + s_2 A_2 = 0$$

$$\begin{bmatrix} 1 & 1 \\ -58.579 & -341.421 \end{bmatrix} \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 4 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} A_1 \\ A_2 \end{bmatrix} = \begin{bmatrix} 4.829 \\ -0.829 \end{bmatrix}, i_{Lf} = 0 \text{ A}$$

$$i_s(t) = 4 u(-t), R = 25 \Omega, L = 500 \text{ mH}, C = 100 \mu\text{F}$$

