

# Solution of ECE 300 Test 13 S09

1. In the partial circuit below, the voltages can be written in terms of the inductances, mutual inductances and the currents. Fill in the coefficient matrix below with numerical magnitudes and angles in degrees.

$$V_1 = j40I_1 - j30I_2 + j50I_3$$


$$V_2 = j80I_2 - j30I_1 - j60I_3$$

$$V_3 = j100I_3 + j50I_1 - j60I_2$$

$$\begin{bmatrix} 40\angle 90^\circ & 30\angle -90^\circ & 50\angle 90^\circ \\ 30\angle -90^\circ & 80\angle 90^\circ & 60\angle -90^\circ \\ 50\angle 90^\circ & 60\angle -90^\circ & 100\angle 90^\circ \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$


$$L_1 = 2\text{ H} , L_2 = 4\text{ H} , L_3 = 5\text{ H} , \omega = 20$$
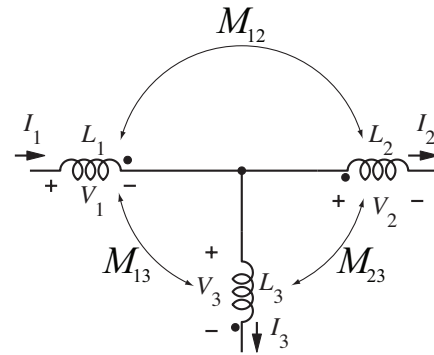
$$M_{12} = 1.5\text{ H} , M_{13} = 2.5\text{ H} , M_{23} = 3\text{ H}$$



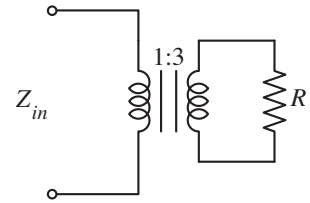2. In the circuit below, if  $R = 15$  and  $\omega = 377$  and the transformer is ideal, what is the numerical value of  $Z_{in}$  ?


Input resistance on the primary (the left side) of the transformer is  $Z_{in2} = (1/3)^2 \times 15\Omega = 1.667\Omega$ .



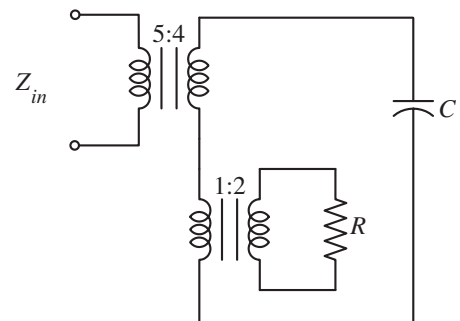3. In the circuit below, the transformers are both ideal,  $R = 20\Omega$ ,  $C = 20\mu\text{F}$  and  $\omega = 377$ . Find the numerical value of  $Z_{in}$ .


Input resistance on the primary (the left side) of the lower transformer is  $Z_{in2} = (1/2)^2 \times 20\Omega = 5\Omega$ . Therefore the load on the secondary (the right side) of the upper transformer is  $Z_{L1} = \frac{1}{j377 \times 20 \times 10^{-6}} + 5 = 5 - j132.63 = 132.72\angle -87.84^\circ \Omega$ . Then the input impedance of the upper transformer is

$$Z_{in1} = (5/4)^2 (132.72\angle -87.84^\circ \Omega) = 7.8125 - j207.23 = 207.38\angle -87.84^\circ$$



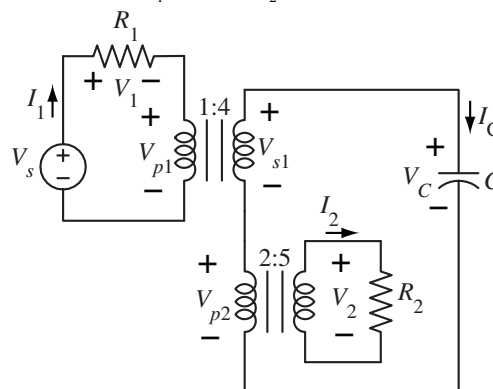4. In the circuit below, the transformers are both ideal.

$$V_s = 120\angle 0^\circ \text{ rms}, R_1 = 10\Omega, R_2 = 50\Omega, C = 80\mu\text{F}, \omega = 377$$



Find the following numerical values: (Be sure KVL is satisfied for all closed loops in the circuit.)

The input impedance of the lower transformer on the primary side (the left side) = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $\Omega$

The load impedance on the secondary of the upper transformer (the right side) = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $\Omega$

The input impedance of the upper transformer on the primary side (the left side) = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $\Omega$

The current  $I_1$  flowing out of the voltage source = \_\_\_\_\_  $\angle$  \_\_\_\_\_ A rms

The voltage  $V_1$  across the resistor  $R_1$  = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Vrms

The voltage  $V_{p1}$  across the primary of the upper transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Vrms

The voltage  $V_{s1}$  across the secondary of the upper transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Vrms

The current  $I_C$  = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Arms

The voltage  $V_C$  across the capacitor = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Vrms

The current  $I_2$  = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Arms

The voltage  $V_2$  across the secondary of the lower transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Vrms

The voltage  $V_{p2}$  across the primary of the lower transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_ Vrms

Input resistance on the primary (the left side) of the lower transformer is  $Z_{in2} = (2/5)^2 \times 50\Omega = 8\Omega$ . Therefore the load on the secondary (the right side) of the upper transformer is  $Z_{L1} = \frac{1}{j377 \times 80 \times 10^{-6}} + 8 = 8 - j33.157 = 34.11\angle -76.43^\circ \Omega$ . Then the input impedance of the upper transformer is

$$Z_{in1} = (1/4)^2 (34.11\angle -76.43^\circ \Omega) = 0.5 - j2.072 = 2.1317\angle -76.44^\circ$$

The current from the voltage source is  $I_1 = \frac{V_s}{R_1 + Z_{in1}} = \frac{120\angle 0^\circ \text{ Vrms}}{10 + 0.5 - j2.072 \Omega} = 11 + j2.17 = 11.212\angle 11.16^\circ$ . The

voltage across  $R_1$  is  $V_1 = I_1 R_1 = 11.212\angle 11.16^\circ \times 10\Omega = 112.12\angle 11.16^\circ$ . The voltage across the primary of the upper transformer is  $V_{p1} = 120\angle 0^\circ - 112.12\angle 11.16^\circ = 23.9\angle -65.27^\circ$ . The voltage across the secondary of the upper transformer is  $V_{s1} = V_{p1} \times 4 = 95.6\angle -65.27^\circ$ . The current through the capacitor is the secondary current of the upper transformer,  $I_C = 11.212\angle 11.16^\circ / 4 = 2.803\angle 11.16^\circ$  and this is also the primary current of the lower

transformer. The voltage  $V_C$  across the capacitor is  $V_C = 2.803\angle 11.16^\circ \times \frac{1}{j377 \times 80 \times 10^{-6}} = 92.94\angle -78.84^\circ$ .

The current  $I_2$  is the secondary current of the lower transformer and is

$I_2 = -I_C \times (2/5) = -2.803 \angle 11.16^\circ \times 2/5 = 1.1212 \angle -168.84^\circ$ . The voltage  $V_2$  across the secondary of the lower transformer is  $V_2 = 1.1212 \angle -168.84^\circ \times 50 = 56.06 \angle -168.84^\circ$ . The voltage across the primary of the lower transformer is  $V_{p2} = 56.06 \angle -168.84^\circ \times (2/5) = 22.424 \angle -168.84^\circ$

## Solution of ECE 300 Test 13 S09

1. In the partial circuit below, the voltages can be written in terms of the inductances, mutual inductances and the currents. Fill in the coefficient matrix below with numerical magnitudes and angles in degrees.

$$V_1 = j60I_1 - j45I_2 + j75I_3$$


$$V_2 = j120I_2 - j45I_1 - j90I_3$$

$$V_3 = j150I_3 + j75I_1 - j90I_2$$

$$\begin{bmatrix} 60\angle 90^\circ & 45\angle -90^\circ & 75\angle 90^\circ \\ 45\angle -90^\circ & 120\angle 90^\circ & 90\angle -90^\circ \\ 75\angle 90^\circ & 90\angle -90^\circ & 150\angle 90^\circ \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$


$$L_1 = 2\text{ H} , L_2 = 4\text{ H} , L_3 = 5\text{ H} , \omega = 30$$
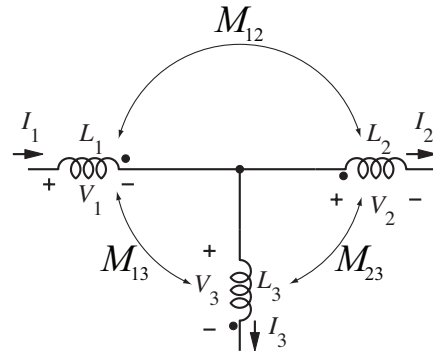
$$M_{12} = 1.5\text{ H} , M_{13} = 2.5\text{ H} , M_{23} = 3\text{ H}$$



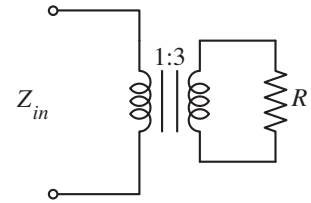2. In the circuit below, if  $R = 25$  and  $\omega = 377$  and the transformer is ideal, what is the numerical value of  $Z_{in}$  ?


Input resistance on the primary (the left side) of the transformer is  $Z_{in2} = (1/3)^2 \times 25\Omega = 2.778\Omega$ .



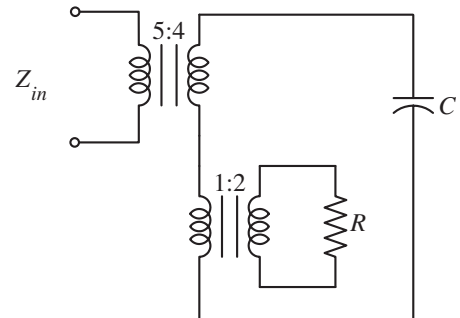3. In the circuit below, the transformers are both ideal,  $R = 30\Omega$ ,  $C = 20\mu\text{F}$  and  $\omega = 377$ . Find the numerical value of  $Z_{in}$ .


Input resistance on the primary (the left side) of the lower transformer is  $Z_{in2} = (1/2)^2 \times 30\Omega = 7.5\Omega$ . Therefore the load on the secondary (the right side) of the upper transformer is  $Z_{L1} = \frac{1}{j377 \times 20 \times 10^{-6}} + 7.5 = 7.5 - j132.63 = 132.84\angle -86.76^\circ \Omega$ . Then the input impedance of the upper transformer is

$$Z_{in1} = (5/4)^2 (132.84\angle -86.76^\circ \Omega) = 11.72 - j207.23 = 207.56\angle -86.76^\circ$$



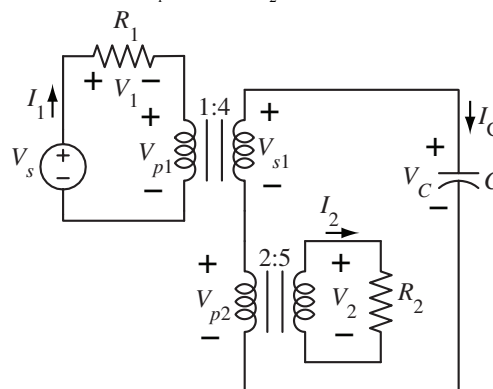4. In the circuit below, the transformers are both ideal.

$$V_s = 120\angle 0^\circ \text{ rms}, R_1 = 10\Omega, R_2 = 30\Omega, C = 80\mu\text{F}, \omega = 377$$



Find the following numerical values: (Be sure KVL is satisfied for all closed loops in the circuit.)

The input impedance of the lower transformer on the primary side (the left side) = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$

The load impedance on the secondary of the upper transformer (the right side) = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$

The input impedance of the upper transformer on the primary side (the left side) = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$

The current  $I_1$  flowing out of the voltage source = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  A rms

The voltage  $V_1$  across the resistor  $R_1$  = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Vrms

The voltage  $V_{p1}$  across the primary of the upper transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Vrms

The voltage  $V_{s1}$  across the secondary of the upper transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Vrms

The current  $I_C$  = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Arms

The voltage  $V_C$  across the capacitor = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Vrms

The current  $I_2$  = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Arms

The voltage  $V_2$  across the secondary of the lower transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Vrms

The voltage  $V_{p2}$  across the primary of the lower transformer = \_\_\_\_\_  $\angle$  \_\_\_\_\_  $^\circ$  Vrms

Input resistance on the primary (the left side) of the lower transformer is  $Z_{in2} = (2/5)^2 \times 30\Omega = 4.8\Omega$ . Therefore the load on the secondary (the right side) of the upper transformer is  $Z_{L1} = \frac{1}{j377 \times 80 \times 10^{-6}} + 4.8 = 4.8 - j33.5 = 33.5\angle -81.76^\circ \Omega$ . Then the input impedance of the upper transformer is

$$Z_{in1} = (1/4)^2 (33.5\angle -81.76^\circ \Omega) = 0.3 - j2.07 = 2.09\angle -81.76^\circ$$

The current from the voltage source is  $I_1 = \frac{V_s}{R_1 + Z_{in1}} = \frac{120\angle 0^\circ \text{ Vrms}}{10 + 0.3 - j2.07 \Omega} = 11.197 + j2.253 = 11.422\angle 11.38^\circ$ .

The voltage across  $R_1$  is  $V_1 = I_1 R_1 = 11.422\angle 11.38^\circ \times 10\Omega = 114.216\angle 11.38^\circ$ . The voltage across the primary of the upper transformer is  $V_{p1} = 120\angle 0^\circ - 114.216\angle 11.38^\circ = 23.92\angle -70.39^\circ$ . The voltage across the secondary of the upper transformer is  $V_{s1} = V_{p1} \times 4 = 95.66\angle -70.39^\circ$ . The current through the capacitor is the secondary current of the upper transformer,  $I_C = 11.42\angle 11.38^\circ / 4 = 2.855\angle 11.38^\circ$  and this is also the primary current of the lower transformer. The voltage  $V_C$  across the capacitor is

$V_C = 2.855\angle 11.38^\circ \times \frac{1}{j377 \times 80 \times 10^{-6}} = 94.68\angle -78.62^\circ$ . The current  $I_2$  is the secondary current of the lower

transformer and is  $I_2 = -I_C \times (2/5) = -2.855 \angle 11.38^\circ \times 2/5 = 1.142 \angle -168.62^\circ$ . The voltage  $V_2$  across the secondary of the lower transformer is  $V_2 = 1.142 \angle -168.62^\circ \times 30 = 34.26 \angle -168.62^\circ$ . The voltage across the primary of the lower transformer is  $V_{p2} = 34.26 \angle -168.62^\circ \times (2/5) = 13.71 \angle -168.62^\circ$