


Solution of ECE 202 Test 6 S13

With reference to the circuit below, fill in the blanks in the mesh equations with correct numerical magnitudes and angles. (As usual, magnitudes must be non-negative and angles should be in the range -180° to $+180^\circ$.)

$$\begin{array}{l} \text{Mesh 2} \rightarrow \\ \text{Mesh 3} \rightarrow \\ \text{Auxiliary} \rightarrow \end{array} \left[\begin{array}{ccc} \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ 1 & 0 & 0 \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4\angle 0^\circ \end{bmatrix}$$

$$I_s = 4\angle 0^\circ \text{ A}, L_1 = 2.5 \text{ H}, L_2 = 4 \text{ H}, M = 2 \text{ H}$$
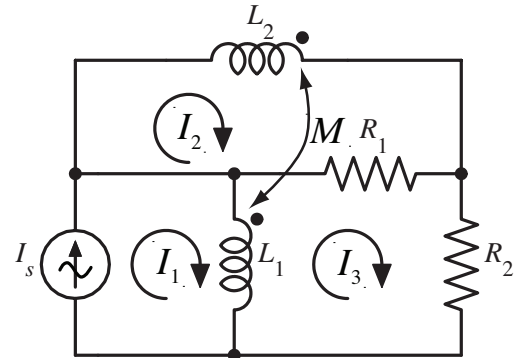
$$R_1 = 240\Omega, R_2 = 350\Omega, \omega = 200 \text{ s}^{-1}$$



$$j\omega L_2 I_2 - j\omega M(I_1 - I_3) + R_1(I_2 - I_3) = 0$$

$$j\omega L_1(I_3 - I_2) + j\omega M I_2 + R_1(I_3 - I_2) + R_2 I_3 = 0$$

$$I_1 = I_s$$

$$\begin{bmatrix} -j\omega M & j\omega L_2 + R_1 & j\omega M - R_1 \\ -j\omega L_1 & j\omega M - R_1 & j\omega L_1 + R_1 + R_2 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} -j400 & j800 + 240 & j400 - 240 \\ -j500 & j400 - 240 & j500 + 590 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4 \end{bmatrix}$$

$$\begin{array}{l} \text{Mesh 2} \rightarrow \\ \text{Mesh 3} \rightarrow \\ \text{Auxiliary} \rightarrow \end{array} \left[\begin{array}{ccc} 400\angle -90^\circ & 835\angle 73.3^\circ & 466.48\angle 120.96^\circ \\ 500\angle -90^\circ & 466.48\angle 120.96^\circ & 773.37\angle 40.28^\circ \\ 1 & 0 & 0 \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4\angle 0^\circ \end{bmatrix}$$


Solution of ECE 202 Test 6 S13

With reference to the circuit below, fill in the blanks in the mesh equations with correct numerical magnitudes and angles. (As usual, magnitudes must be non-negative and angles should be in the range -180° to $+180^\circ$.)

$$\begin{array}{l} \text{Mesh 2} \rightarrow \\ \text{Mesh 3} \rightarrow \\ \text{Auxiliary} \rightarrow \end{array} \left[\begin{array}{ccc} \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ 1 & 0 & 0 \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4\angle 0^\circ \end{bmatrix}$$

$$I_s = 4\angle 0^\circ \text{ A}, L_1 = 3.5 \text{ H}, L_2 = 7 \text{ H}, M = 4 \text{ H}$$
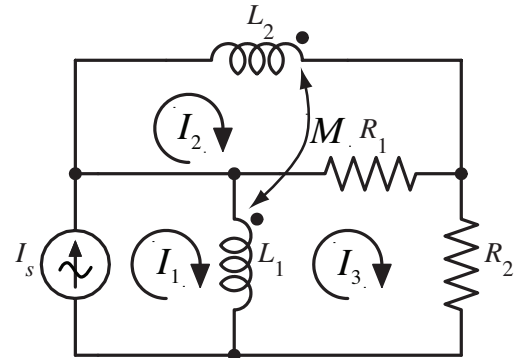
$$R_1 = 280\Omega, R_2 = 310\Omega, \omega = 200 \text{ s}^{-1}$$



$$j\omega L_2 I_2 - j\omega M(I_1 - I_3) + R_1(I_2 - I_3) = 0$$

$$j\omega L_1(I_3 - I_2) + j\omega M I_2 + R_1(I_3 - I_2) + R_2 I_3 = 0$$

$$I_1 = I_s$$

$$\begin{bmatrix} -j\omega M & j\omega L_2 + R_1 & j\omega M - R_1 \\ -j\omega L_1 & j\omega M - R_1 & j\omega L_1 + R_1 + R_2 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} -j800 & j1400 + 280 & j800 - 280 \\ -j700 & j800 - 280 & j700 + 590 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4 \end{bmatrix}$$

$$\begin{array}{l} \text{Mesh 2} \rightarrow \\ \text{Mesh 3} \rightarrow \\ \text{Auxiliary} \rightarrow \end{array} \left[\begin{array}{ccc} 800\angle -90^\circ & 1427.73\angle 78.69^\circ & 847.58\angle 109.29^\circ \\ 700\angle -90^\circ & 847.58\angle 109.29^\circ & 915.48\angle 49.87^\circ \\ 1 & 0 & 0 \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4\angle 0^\circ \end{bmatrix}$$


Solution of ECE 202 Test 6 S13

With reference to the circuit below, fill in the blanks in the mesh equations with correct numerical magnitudes and angles. (As usual, magnitudes must be non-negative and angles should be in the range -180° to $+180^\circ$.)

$$\begin{array}{l} \text{Mesh 2} \rightarrow \\ \text{Mesh 3} \rightarrow \\ \text{Auxiliary} \rightarrow \end{array} \left[\begin{array}{ccc} \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ 1 & 0 & 0 \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4\angle 0^\circ \end{bmatrix}$$

$$I_s = 4\angle 0^\circ \text{ A}, L_1 = 1.5 \text{ H}, L_2 = 3 \text{ H}, M = 1 \text{ H}$$
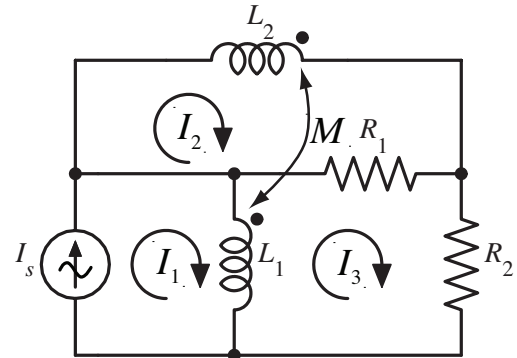
$$R_1 = 340\Omega, R_2 = 250\Omega, \omega = 200 \text{ s}^{-1}$$



$$j\omega L_2 I_2 - j\omega M(I_1 - I_3) + R_1(I_2 - I_3) = 0$$

$$j\omega L_1(I_3 - I_2) + j\omega M I_2 + R_1(I_3 - I_2) + R_2 I_3 = 0$$

$$I_1 = I_s$$

$$\begin{bmatrix} -j\omega M & j\omega L_2 + R_1 & j\omega M - R_1 \\ -j\omega L_1 & j\omega M - R_1 & j\omega L_1 + R_1 + R_2 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ I_s \end{bmatrix}$$

$$\begin{bmatrix} -j200 & j600 + 340 & j200 - 340 \\ -j300 & j200 - 340 & j300 + 590 \\ 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4 \end{bmatrix}$$

$$\begin{array}{l} \text{Mesh 2} \rightarrow \\ \text{Mesh 3} \rightarrow \\ \text{Auxiliary} \rightarrow \end{array} \left[\begin{array}{ccc} 200\angle -90^\circ & 689.64\angle 60.46^\circ & 394.46\angle 149.53^\circ \\ 300\angle -90^\circ & 394.46\angle 149.53^\circ & 661.89\angle 26.95^\circ \\ 1 & 0 & 0 \end{array} \right] \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 4\angle 0^\circ \end{bmatrix}$$