


Solution of ECE 202 Test 7 S13

(14 pts) Using the relations between voltages and currents for ideal transformers, it is possible to write a system of three equations and three unknowns for the circuit below. Fill in the blanks with correct numbers.

$$\begin{bmatrix} \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & 0 \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & 0 & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$V_g = 120 \angle 0^\circ \text{ Vrms}, R_p = 50 \Omega, R_s = 240 \Omega$$
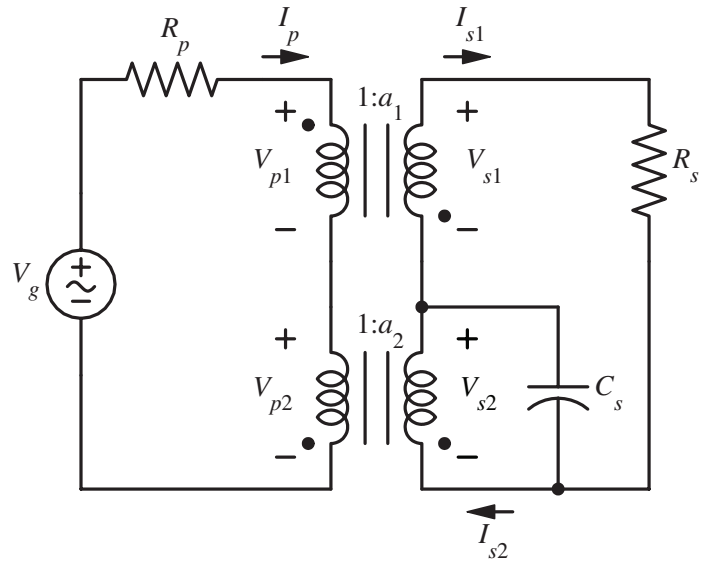
$$C_s = 320 \mu\text{F}, a_1 = 3, a_2 = 0.75, \omega = 200 \text{ s}^{-1}$$



$$-V_g + R_p I_p + V_{p1} + V_{p2} = 0$$

$$-V_{s1} + R_s I_{s1} + \frac{1}{j\omega C_s} (I_{s1} - I_{s2}) = 0$$

$$-V_{s2} + \frac{1}{j\omega C_s} (I_{s2} - I_{s1}) = 0$$

$$\begin{bmatrix} R_p & 1 & 1 \\ \frac{R_s}{-a_1} + \frac{1}{j\omega C_s} \left(\frac{1}{-a_1} - \frac{1}{a_2} \right) & a_1 & 0 \\ \frac{1}{j\omega C_s} \left(\frac{1}{a_2} - \frac{1}{-a_1} \right) & 0 & -a_2 \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 50 & 1 & 1 \\ -\frac{240}{3} + \frac{1}{j200 \times 320 \times 10^{-6}} \left(-\frac{1}{3} - \frac{1}{0.75} \right) & 3 & 0 \\ \frac{1}{j200 \times 320 \times 10^{-6}} \left(\frac{1}{0.75} + \frac{1}{3} \right) & 0 & -0.75 \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 50 \angle 0^\circ & 1 \angle 0^\circ & 1 \angle 0^\circ \\ 84.1319 \angle 161.97^\circ & 3 \angle 0^\circ & 0 \\ 26.0417 \angle -90^\circ & 0 & 0.75 \angle 180^\circ \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$


Solution of ECE 202 Test 7 S13

(14 pts) Using the relations between voltages and currents for ideal transformers, it is possible to write a system of three equations and three unknowns for the circuit below. Fill in the blanks with correct numbers.

$$\begin{bmatrix} \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & 0 \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & 0 & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$V_g = 120 \angle 0^\circ \text{ Vrms}, R_p = 75 \Omega, R_s = 120 \Omega$$
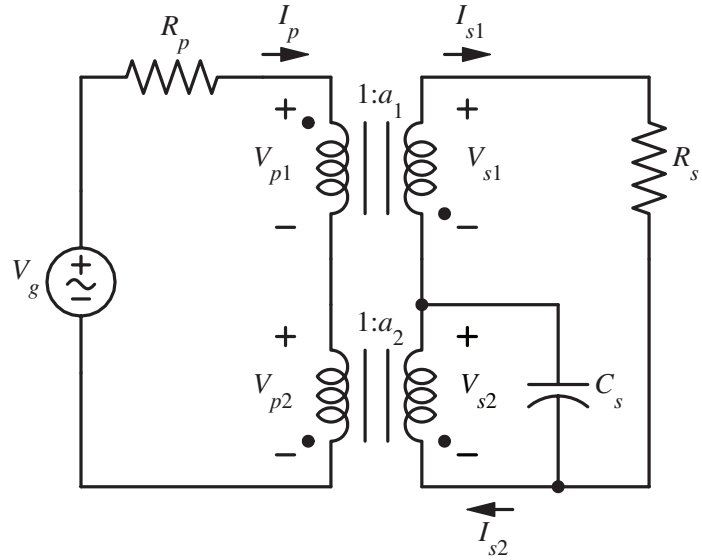
$$C_s = 240 \mu\text{F}, a_1 = 2, a_2 = 0.5, \omega = 100 \text{ s}^{-1}$$



$$-V_g + R_p I_p + V_{p1} + V_{p2} = 0$$

$$-V_{s1} + R_s I_{s1} + \frac{1}{j\omega C_s} (I_{s1} - I_{s2}) = 0$$

$$-V_{s2} + \frac{1}{j\omega C_s} (I_{s2} - I_{s1}) = 0$$

$$\begin{bmatrix} R_p & 1 & 1 \\ \frac{R_s}{-a_1} + \frac{1}{j\omega C_s} \left(\frac{1}{-a_1} - \frac{1}{a_2} \right) & a_1 & 0 \\ \frac{1}{j\omega C_s} \left(\frac{1}{a_2} - \frac{1}{-a_1} \right) & 0 & -a_2 \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 75 & 1 & 1 \\ -\frac{120}{2} + \frac{1}{j100 \times 240 \times 10^{-6}} \left(\frac{1}{-2} - \frac{1}{0.5} \right) & 2 & 0 \\ \frac{1}{j100 \times 240 \times 10^{-6}} \left(\frac{1}{0.5} - \frac{1}{-2} \right) & 0 & -0.5 \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 75 \angle 0^\circ & 1 \angle 0^\circ & 1 \angle 0^\circ \\ 120.211 \angle 119.942^\circ & 2 \angle 0^\circ & 0 \\ 104.167 \angle -90^\circ & 0 & 0.5 \angle 180^\circ \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$


Solution of ECE 202 Test 7 S13

(14 pts) Using the relations between voltages and currents for ideal transformers, it is possible to write a system of three equations and three unknowns for the circuit below. Fill in the blanks with correct numbers.

$$\begin{bmatrix} \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & 0 \\ \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ & 0 & \underline{\hspace{1cm}} \angle \underline{\hspace{1cm}}^\circ \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$

$$V_g = 120 \angle 0^\circ \text{ Vrms}, R_p = 100 \Omega, R_s = 360 \Omega$$
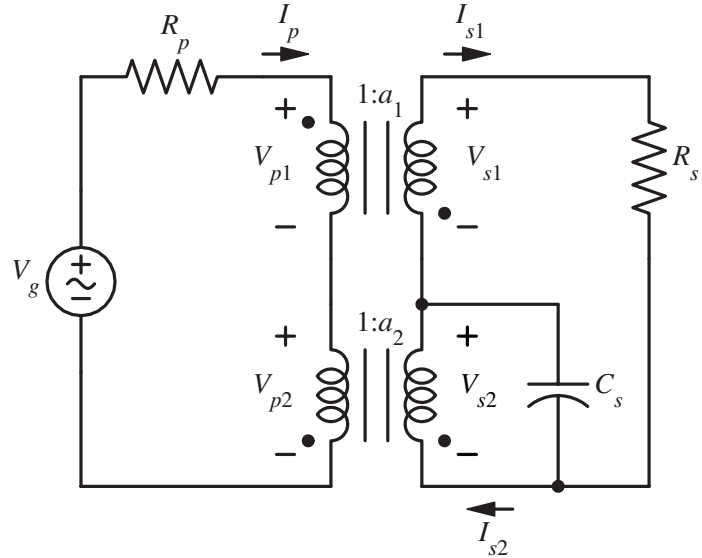
$$C_s = 400 \mu\text{F}, a_1 = 4, a_2 = 0.25, \omega = 300 \text{ s}^{-1}$$



$$-V_g + R_p I_p + V_{p1} + V_{p2} = 0$$

$$-V_{s1} + R_s I_{s1} + \frac{1}{j\omega C_s} (I_{s1} - I_{s2}) = 0$$

$$-V_{s2} + \frac{1}{j\omega C_s} (I_{s2} - I_{s1}) = 0$$

$$\begin{bmatrix} R_p & 1 & 1 \\ \frac{R_s}{-a_1} + \frac{1}{j\omega C_s} \left(\frac{1}{-a_1} - \frac{1}{a_2} \right) & a_1 & 0 \\ \frac{1}{j\omega C_s} \left(\frac{1}{a_2} - \frac{1}{-a_1} \right) & 0 & -a_2 \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 100 & 1 & 1 \\ -\frac{360}{4} + \frac{1}{j300 \times 400 \times 10^{-6}} \left(\frac{1}{-4} - \frac{1}{0.25} \right) & 4 & 0 \\ \frac{1}{j300 \times 400 \times 10^{-6}} \left(\frac{1}{0.25} - \frac{1}{-4} \right) & 0 & -0.25 \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} V_g \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 100 \angle 0^\circ & 1 \angle 0^\circ & 1 \angle 0^\circ \\ 96.718 \angle 158.519^\circ & 4 \angle 0^\circ & 0 \\ 35.4167 \angle -90^\circ & 0 & 0.25 \angle 180^\circ \end{bmatrix} \begin{bmatrix} I_p \\ V_{p1} \\ V_{p2} \end{bmatrix} = \begin{bmatrix} 120 \angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$