

Solution of EECS 300 Test 11 F08

1. With reference to the circuit below, let

$$I = 20\angle 0^\circ \text{ operating at } \omega = 1000, R = 50 \Omega, C = 30 \mu\text{F}, L = 80 \text{ mH}$$

and find the following numerical values.

- (a) $|V_C| = \text{_____ V}, \angle V_C = \text{_____}^\circ$
- (b) $|V_R| = \text{_____ V}, \angle V_R = \text{_____}^\circ$
- (c) $|V_L| = \text{_____ V}, \angle V_L = \text{_____}^\circ$
- (d) $|I_C| = \text{_____ A}, \angle I_C = \text{_____}^\circ$
- (e) $|I_L| = \text{_____ A}, \angle I_L = \text{_____}^\circ$
- (f) The average power supplied by the current source $P_s = \text{_____ W}$
- (g) The average power absorbed by the resistor $P_R = \text{_____ W}$
- (h) The complex power absorbed by the current source $\mathbf{S}_s = \text{_____} \angle \text{_____}^\circ \text{ VA}$
- (i) The complex power absorbed by the capacitor $\mathbf{S}_C = \text{_____} \angle \text{_____}^\circ \text{ VA}$
- (j) The complex power absorbed by the resistor $\mathbf{S}_R = \text{_____} \angle \text{_____}^\circ \text{ VA}$
- (k) The complex power absorbed by the inductor $\mathbf{S}_L = \text{_____} \angle \text{_____}^\circ \text{ VA}$

The impedance driven by the current source is

$$Z = (1/j\omega C) \parallel (R + j\omega L) = \frac{(1/j0.03)(50 + j80)}{1/j0.03 + 50 + j80} = \frac{-j33.33(50 + j80)}{-j33.33 + 50 + j80}$$

$$Z = \frac{-j1666.7 + 2666.7}{50 + j46.67} = 45.98 \angle -75.03^\circ \Omega$$

The voltage across the current source (and the capacitor) is

$$V_s = IZ = 20\angle 0^\circ \times 45.98 \angle -75.03^\circ = 919.6 \angle -75.03^\circ \text{ V}$$

The current through the capacitor is

$$I_C = V_s \times j\omega C = 919.6 \angle -75.03^\circ \times j0.03 = 27.58 \angle 14.96^\circ \text{ A}$$

The current through the resistor and inductor is

$$I_L = I - I_C = 20\angle 0^\circ - 27.58 \angle 14.96^\circ = 9.747 \angle -133.03^\circ \text{ A}$$

The voltage across the resistor is $V_R = I_L R = 487.37 \angle -133.03^\circ \text{ V}$.

The voltage across the inductor is $V_L = I_L \times j\omega L = 779.79 \angle -43.03^\circ \text{ V}$.

The average power supplied by the current source is $P_s = (|V_s| |I| / 2) \cos(\angle V_s - \angle I) = 2375.3 \text{ W}$

The average power absorbed by the resistor is $P_R = |I_R|^2 R / 2 = 2375.3 \text{ W}$

The complex power absorbed by the source is

$$\mathbf{S}_s = \mathbf{V}_{\text{eff}} \mathbf{I}_{\text{eff}}^* = -\frac{919.6}{\sqrt{2}} \angle -75.03^\circ \times \frac{20}{\sqrt{2}} \angle 0^\circ = 9196 \angle 104.96^\circ \text{ VA}$$

The complex power absorbed by the capacitor is

$$\mathbf{S}_C = \mathbf{V}_{\text{eff}} \mathbf{I}_{\text{eff}}^* = \frac{919.6}{\sqrt{2}} \angle -75.03^\circ \times \frac{27.58}{\sqrt{2}} \angle -14.96^\circ = 12,684 \angle -90^\circ \text{ VA}$$


The complex power absorbed by the resistor is

$$\mathbf{S}_R = \mathbf{V}_{\text{eff}} \mathbf{I}_{\text{eff}}^* = \frac{487.37}{\sqrt{2}} \angle -1333.03^\circ \times \frac{9.747}{\sqrt{2}} \angle 133.03^\circ = 2375.3 \angle 0^\circ \text{ VA}$$

The complex power absorbed by the inductor is

$$\mathbf{S}_L = \mathbf{V}_{\text{eff}} \mathbf{I}_{\text{eff}}^* = \frac{779.79}{\sqrt{2}} \angle -43.03^\circ \times \frac{9.747}{\sqrt{2}} \angle 133.03^\circ = 3800.5 \angle 90^\circ \text{ VA}$$

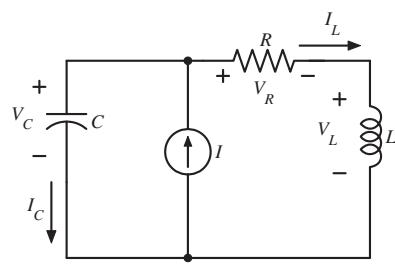The absorbed complex powers add to zero as they should.



2. With reference to the circuit below, let

$$V_s = 120\angle 0^\circ \text{ rms operating at } \omega = 377, R = 20 \text{ k}\Omega, C = 90 \text{ nF}$$

Find the numerical average power delivered to

- (a) the resistor
- (b) the dependent current source
- (c) Find the numerical instantaneous power delivered by the dependent voltage source at time $t = 10 \text{ ms}$.

$$I_R = V_s / R = \frac{120\angle 0^\circ \text{ Vrms}}{20,000 \Omega} = 6\angle 0^\circ \text{ mA rms} \Rightarrow P_R = I_{\text{eff}}^2 R = (6 \times 10^{-3} \text{ A})^2 20,000 \Omega = 0.72 \text{ W}$$

$$V_C \times j\omega C + 0.5I_R = 0$$

$$V_C = \frac{-0.5V_s}{j\omega RC} = -\frac{-60\angle 0^\circ \text{ Vrms}}{j(377 \text{ rad/s})(20,000 \Omega)(90 \times 10^{-9} \text{ F})} = j88.417 \text{ Vrms}$$


$$V_{DS} = V_s - V_C = 120\angle 0^\circ \text{ Vrms} - (j88.417 \text{ Vrms}) = 149.06\angle 143.62^\circ \text{ Vrms (positive on left)}$$

$$I_{DS} = 0.5I_R = 3\angle 0^\circ \text{ mA rms}$$

$$P_{DS} = -|V_{DS}||I_{DS}|\cos(143.62^\circ) = -149.06 \times 0.003 \times (-0.805) = 0.36 \text{ W}$$

$$p_{DS}(t) = 149.06\sqrt{2} \cos(377t + 143.62^\circ) 0.003\sqrt{2} \cos(377t) \text{ W}$$
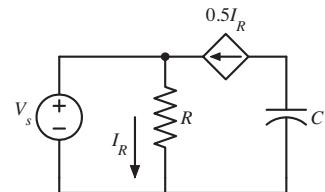
$$p_{DS}(10 \text{ ms}) = 149.06\sqrt{2} \cos(377 \times 10 \text{ ms} + 143.62^\circ) 0.003\sqrt{2} \cos(377 \times 10 \text{ ms}) = -0.7235 \text{ W}$$



Solution of EECS 300 Test 11 F08

1. With reference to the circuit below, let

$$I = 8\angle 0^\circ \text{ operating at } \omega = 1000, R = 50 \Omega, C = 30 \mu\text{F}, L = 80 \text{ mH}$$

and find the following numerical values.

- (a) $|V_C| = \text{_____ V}, \angle V_C = \text{_____ }^\circ$
- (b) $|V_R| = \text{_____ V}, \angle V_R = \text{_____ }^\circ$
- (c) $|V_L| = \text{_____ V}, \angle V_L = \text{_____ }^\circ$
- (d) $|I_C| = \text{_____ A}, \angle I_C = \text{_____ }^\circ$
- (e) $|I_L| = \text{_____ A}, \angle I_L = \text{_____ }^\circ$
- (f) The average power supplied by the current source $P_s = \text{_____ W}$
- (g) The average power absorbed by the resistor $P_R = \text{_____ W}$
- (h) The complex power absorbed by the current source $S_s = \text{_____ } \angle \text{_____ }^\circ \text{ VA}$
- (i) The complex power absorbed by the capacitor $S_C = \text{_____ } \angle \text{_____ }^\circ \text{ VA}$
- (j) The complex power absorbed by the resistor $S_R = \text{_____ } \angle \text{_____ }^\circ \text{ VA}$
- (k) The complex power absorbed by the inductor $S_L = \text{_____ } \angle \text{_____ }^\circ \text{ VA}$

The impedance driven by the current source is

$$Z = (1/j\omega C) \parallel (R + j\omega L) = \frac{(1/j0.03)(50 + j80)}{1/j0.03 + 50 + j80} = \frac{-j33.33(50 + j80)}{-j33.33 + 50 + j80}$$

$$Z = \frac{-j1666.7 + 2666.7}{50 + j46.67} = 45.98 \angle -75.03^\circ \Omega$$

The voltage across the current source (and the capacitor) is

$$V_s = IZ = 8\angle 0^\circ \times 45.98 \angle -75.03^\circ = 367.8 \angle -75.03^\circ \text{ V}$$

The current through the capacitor is

$$I_C = V_s \times j\omega C = 367.8 \angle -75.03^\circ \times j0.03 = 11.032 \angle 14.96^\circ \text{ A}$$

The current through the resistor and inductor is

$$I_L = I - I_C = 8\angle 0^\circ - 11.032 \angle 14.96^\circ = 3.899 \angle -133.03^\circ \text{ A}$$

The voltage across the resistor is $V_R = I_L R = 194.95 \angle -133.03^\circ \text{ V}$.

The voltage across the inductor is $V_L = I_L \times j\omega L = 311.92 \angle -43.03^\circ \text{ V}$.

The average power supplied by the current source is $P_s = (|V_s| |I| / 2) \cos(\angle V_s - \angle I) = 380 \text{ W}$

The average power absorbed by the resistor is $P_R = |I_R|^2 R / 2 = 380 \text{ W}$

The complex power absorbed by the source is

$$S_s = \mathbf{V}_{\text{eff}} \mathbf{I}_{\text{eff}}^* = -\frac{367.8}{\sqrt{2}} \angle -75.03^\circ \times \frac{8}{\sqrt{2}} \angle 0^\circ = 1471.4 \angle 104.96^\circ \text{ VA}$$

The complex power absorbed by the capacitor is

$$\mathbf{S}_C = \mathbf{V}_{eff} \mathbf{I}_{eff}^* = \frac{367.8}{\sqrt{2}} \angle -75.03^\circ \times \frac{11.03}{\sqrt{2}} \angle -14.96^\circ = 2029.6 \angle -90^\circ \text{ VA}$$


The complex power absorbed by the resistor is

$$\mathbf{S}_R = \mathbf{V}_{eff} \mathbf{I}_{eff}^* = \frac{194.95}{\sqrt{2}} \angle -1333.03^\circ \times \frac{3.899}{\sqrt{2}} \angle 133.03^\circ = 380 \angle 0^\circ \text{ VA}$$

The complex power absorbed by the inductor is

$$\mathbf{S}_L = \mathbf{V}_{eff} \mathbf{I}_{eff}^* = \frac{311.9}{\sqrt{2}} \angle -43.03^\circ \times \frac{3.899}{\sqrt{2}} \angle 133.03^\circ = 608.1 \angle 90^\circ \text{ VA}$$

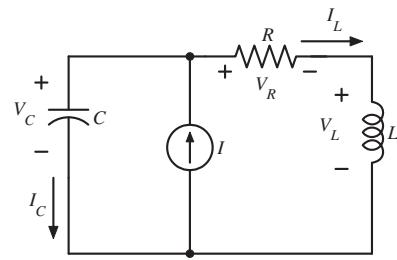The absorbed complex powers add to zero as they should.



2. With reference to the circuit below, let

$$V_s = 90\angle 0^\circ \text{ rms operating at } \omega = 377, R = 20 \text{ k}\Omega, C = 90 \text{ nF}$$

Find the numerical average power delivered to

- (a) the resistor
- (b) the dependent current source
- (c) Find the numerical instantaneous power delivered by the dependent voltage source at time $t = 10 \text{ ms}$.

$$I_R = V_s / R = \frac{90\angle 0^\circ \text{ Vrms}}{20,000 \Omega} = 4.5\angle 0^\circ \text{ mA rms} \Rightarrow P_R = I_{\text{eff}}^2 R = (4.5 \times 10^{-3} \text{ A})^2 20,000 \Omega = 0.405 \text{ W}$$

$$V_C \times j\omega C + 0.5I_R = 0$$

$$V_C = \frac{-0.5V_s}{j\omega RC} = -\frac{-45\angle 0^\circ \text{ Vrms}}{j(377 \text{ rad/s})(20,000 \Omega)(90 \times 10^{-9} \text{ F})} = j66.31 \text{ Vrms}$$

$$V_{DS} = V_s - V_C = 90\angle 0^\circ \text{ Vrms} - (j66.31 \text{ Vrms}) = 111.8\angle 143.62^\circ \text{ Vrms} \text{ (positive on left)}$$

$$I_{DS} = 0.5I_R = 2.25\angle 0^\circ \text{ mA rms}$$

$$P_{DS} = -|V_{DS}||I_{DS}|\cos(143.62^\circ) = -111.8 \times 0.00225 \times (-0.805) = 0.2025 \text{ W}$$

$$p_{DS}(t) = 111.8\sqrt{2} \cos(377t + 143.62^\circ) 0.00225\sqrt{2} \cos(377t) \text{ W}$$

$$p_{DS}(10 \text{ ms}) = 111.8\sqrt{2} \cos(377 \times 10 \text{ ms} + 143.62^\circ) 0.00225\sqrt{2} \cos(377 \times 10 \text{ ms}) = -0.407 \text{ W}$$

