

Solution of EECS 300 Test 9 F08


1. Real physical inductors do not behave exactly like ideal inductors. Their real impedance can be modeled by the circuit below. Let $L = 400 \text{ mH}$, $R = 2 \Omega$, $C = 300 \text{ pF}$. Find the numerical value of the impedance Z_{eq} at $\omega = 90,000$.

$$Z_{eq} = \frac{(j\omega L + R)(1/j\omega C)}{j\omega L + R + 1/j\omega C} = \frac{(j90000 \times 0.4 + 2)(1/j90000 \times 300 \times 10^{-12})}{j90000 \times 0.4 + 2 + 1/j90000 \times 300 \times 10^{-12}}$$

$$Z_{eq} = \frac{(j36000 + 2)(-j37037)}{j36000 + 2 - j37037} = \frac{1.3333 \times 10^9 - j74074}{2 - j1037} = \frac{1.3333 \times 10^9 \angle 0^\circ}{1037 \angle -90^\circ} = 1.2854 \times 10^6 \angle 90^\circ$$

A slightly more accurate result (avoiding some roundoff errors) is
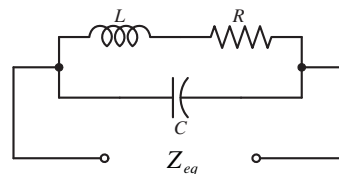
$$Z_{eq} = 2551 + j1.286 \times 10^6 \Omega = 1.286 \times 10^6 \angle 1.569^\circ \Omega = 1.286 \times 10^6 \angle 89.88^\circ \Omega$$



2. Let $i(t) = 120 \cos(\omega t)$, $R = 200 \Omega$, $C = 200 \mu\text{F}$ and $L = 2 \text{ H}$. If $\omega = 377$ and $v_L(t) = A \cos(\omega t + \phi)$, find the numerical values of A and ϕ .


$$Z_{RLC} = \frac{R(j\omega L + 1/j\omega C)}{R + j\omega L + 1/j\omega C} = \frac{200(j377 \times 2 + 1/j377 \times 200 \times 10^{-6})}{200 + j377 \times 2 + 1/j377 \times 200 \times 10^{-6}}$$

$$Z_{RLC} = \frac{200(j754 - j13.3)}{200 + j377 \times 2 + 1/j377 \times 200 \times 10^{-6}} = \frac{200(j754 - j13.3)}{200 + j754 - j13.3}$$

$$Z_{RLC} = \frac{200(j754 - j13.3)}{200 + j754 - j13.3} = \frac{200(j740.7)}{200 + j740.7} = 193.1 \angle 15.11^\circ$$

$$V_L = I Z_{RLC} \frac{j\omega L}{j\omega L + 1/j\omega C} = 120 \angle 0^\circ \times 193.1 \angle 15.11^\circ \times \frac{j754}{j740.7}$$
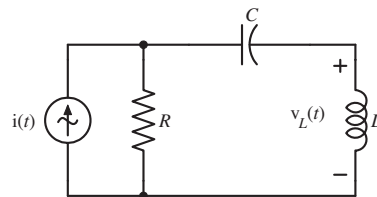
$$V_L = 23,589 \angle 15.11^\circ \Rightarrow v_L(t) = 23,589 \cos(377t + 15.11^\circ)$$



Solution of EECS 300 Test 9 F08


1. Real physical inductors do not behave exactly like ideal inductors. Their real impedance can be modeled by the circuit below. Let $L = 400 \text{ mH}$, $R = 2 \Omega$, $C = 300 \text{ pF}$. Find the numerical value of the impedance Z_{eq} at $\omega = 100,000$.

$$Z_{eq} = \frac{(j\omega L + R)(1/j\omega C)}{j\omega L + R + 1/j\omega C} = \frac{(j100000 \times 0.4 + 2)(1/j100000 \times 300 \times 10^{-12})}{j100000 \times 0.4 + 2 + 1/j100000 \times 300 \times 10^{-12}}$$

$$Z_{eq} = \frac{(j40000 + 2)(-j33333)}{j40000 + 2 - j33333} = \frac{1.3333 \times 10^9 - j66666}{2 + j6667} = \frac{1.3333 \times 10^9 \angle 0^\circ}{6667 \angle 90^\circ} = 2 \times 10^5 \angle -90^\circ$$

A slightly more accurate result (avoiding some roundoff errors) is
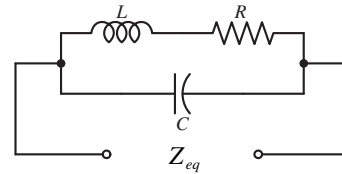
$$Z_{eq} = 50 - j2 \times 10^5 \Omega = 2 \times 10^5 \angle -1.5705^\circ \Omega = 2 \times 10^5 \angle -89.99^\circ \Omega$$



2. Let $i(t) = 120 \cos(\omega t)$, $R = 200 \Omega$, $C = 200 \mu\text{F}$ and $L = 2 \text{ H}$. If $\omega = 200$ and $v_L(t) = A \cos(\omega t + \phi)$, find the numerical values of A and ϕ .

$$Z_{RLC} = \frac{R(j\omega L + 1/j\omega C)}{R + j\omega L + 1/j\omega C} = \frac{200(j200 \times 2 + 1/j200 \times 200 \times 10^{-6})}{200 + j200 \times 2 + 1/j200 \times 200 \times 10^{-6}}$$

$$Z_{RLC} = \frac{200(j400 - j25)}{200 + j400 - j25} = \frac{200(j375)}{200 + j375} = 176.5 \angle 28.07^\circ$$

$$V_L = I Z_{RLC} \frac{j\omega L}{j\omega L + 1/j\omega C} = 120 \angle 0^\circ \times 176.5 \angle 28.07^\circ \times \frac{j400}{j375}$$

$$V_L = 22,592 \angle 28.07^\circ \Rightarrow v_L(t) = 22,592 \cos(377t + 28.07^\circ)$$

