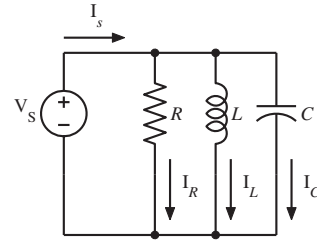


Solution of EECS 300 Test 10 F08

1. In the circuit below let $V_s = 20\angle 0^\circ \text{ V}$, $R = 2 \text{ k}\Omega$, $L = 0.5 \text{ H}$ and $C = 400 \text{ nF}$ with $\omega = 5000 \text{ rad/s}$.

- (a) The magnitude and angle of the phasor current I_R .
- (b) The magnitude and angle of the phasor current I_L .
- (c) The magnitude and angle of the phasor current I_C .
- (d) The magnitude and angle of the phasor current I_s .



$$I_R = \frac{20\angle 0^\circ \text{ V}}{2000\Omega} = 10\angle 0^\circ \text{ mA}$$


$$I_L = \frac{20\angle 0^\circ \text{ V}}{j(5000 \text{ rad/s})(0.5 \text{ H})} = -j8 \text{ mA} = 8\angle -90^\circ \text{ mA}$$

$$I_C = (20\angle 0^\circ \text{ V})(j(5000 \text{ rad/s})(400 \text{ nF})) = j40 \text{ mA} = 40\angle 90^\circ \text{ mA}$$

$$I_s = I_R + I_L + I_C = (10\angle 0^\circ + 8\angle -90^\circ + 40\angle 90^\circ) \text{ mA} = (10 + j32) \text{ mA} = 33.53\angle 72.65^\circ \text{ mA}$$

(continued on next page)

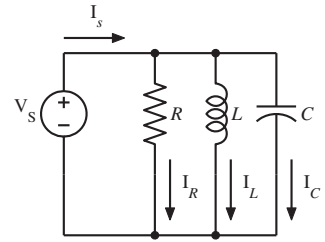- (e) Is the source current leading or lagging the source voltage?
- (e) The power being delivered by the voltage source at time $t = 10 \text{ ms}$.
- (f) The energy stored in the capacitor at time $t = 10 \text{ ms}$.



The source current leads the source voltage by 72.65° .

$$p_s(t) = v_s(t) i_s(t) = [20 \cos(5000t) \text{ V}] [33.53 \cos(5000t + 72.65^\circ) \text{ mA}]$$

$$p_s(t) = 0.6706 \cos(5000t) \cos(5000t + 72.65^\circ) \text{ W}$$

$$p_s(10 \text{ ms}) = 0.6706 \cos(50) \cos(50 + 1.268) \text{ W} = 0.3483 \text{ W}$$

$$e_c(t) = (1/2) C v_c^2(t) = (1/2) (400 \text{ nF}) [20^2 \cos^2(5000t) \text{ V}^2]$$


$$e_c(10 \text{ ms}) = (1/2) (400 \text{ nF}) [400 \cos^2(50) \text{ V}^2] = 74.49 \mu\text{J}$$

2. In the circuit below $R = 10 \text{ k}\Omega$, $L = 50 \text{ mH}$ and $C = 600 \text{ pF}$ with $\omega = 100,000 \text{ rad/s}$ and $I_{RC} = 1\angle 0^\circ \text{ A}$.

(a) Find the magnitude and angle of the phasor voltage V_C .

(b) Find the magnitude and angle of the phasor voltage V_L .

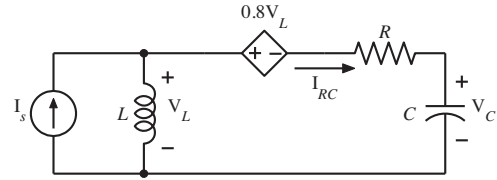(c) Find the magnitude and angle of the phasor current I_s .



$$V_C = I_{RC} \frac{1}{j\omega C} = (1\angle 0^\circ \text{ A}) \frac{1}{j(100,000 \text{ rad/s})(600 \times 10^{-12} \text{ F})} = -j16667 \text{ V} = 16,667 \angle -90^\circ \text{ V}$$

$$-V_L + 0.8V_L + (1\angle 0^\circ \text{ A})(10,000 \Omega) + 16,667 \angle -90^\circ \text{ V} = 0$$

$$-0.2V_L = (-10,000 - 16,667 \angle -90^\circ) \text{ V} \Rightarrow V_L = \frac{-10,000 - 16,667 \angle -90^\circ}{-0.2} \text{ V} = 97,184 \angle -59.04^\circ \text{ V}$$


$$I_L = \frac{V_L}{j\omega L} = \frac{97,184 \angle -59.04^\circ \text{ V}}{j(100,000 \text{ rad/s})(50 \text{ mH})} = 19.44 \angle -149.04^\circ \text{ A} \text{ (flowing downward)}$$

$$I_s = I_{RC} + I_L = (1\angle 0^\circ + 19.44 \angle -149.04^\circ) \text{ A} = 18.586 \angle -147.45^\circ \text{ A}$$

Solution of EECS 300 Test 10 F08

1. In the circuit below let $V_s = 20\angle 0^\circ \text{ V}$, $R = 2 \text{ k}\Omega$, $L = 0.5 \text{ H}$ and $C = 400 \text{ nF}$ with $\omega = 3000 \text{ rad/s}$.

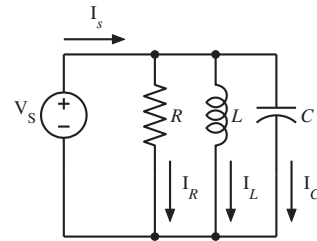- (a) The magnitude and angle of the phasor current I_R .
- (b) The magnitude and angle of the phasor current I_L .
- (c) The magnitude and angle of the phasor current I_C .
- (d) The magnitude and angle of the phasor current I_s .



$$I_R = \frac{20\angle 0^\circ \text{ V}}{2000\Omega} = 10\angle 0^\circ \text{ mA}$$


$$I_L = \frac{20\angle 0^\circ \text{ V}}{j(3000 \text{ rad/s})(0.5 \text{ H})} = -j13.3 \text{ mA} = 13.3\angle -90^\circ \text{ mA}$$

$$I_C = (20\angle 0^\circ \text{ V})(j(3000 \text{ rad/s})(400 \text{ nF})) = j24 \text{ mA} = 24\angle 90^\circ \text{ mA}$$

$$I_s = I_R + I_L + I_C = (10\angle 0^\circ + 13.3\angle -90^\circ + 24\angle 90^\circ) \text{ mA} = (10 + j10.7) \text{ mA} = 14.65\angle 46.94^\circ \text{ mA}$$

(continued on next page)

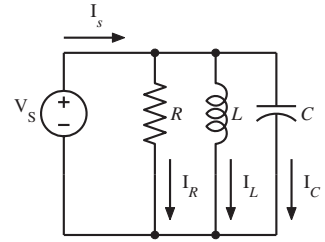- (e) Is the source current leading or lagging the source voltage?
- (e) The power being delivered by the voltage source at time $t = 10 \text{ ms}$.
- (f) The energy stored in the capacitor at time $t = 10 \text{ ms}$.



The source current leads the source voltage by 46.94° .

$$p_s(t) = v_s(t) i_s(t) = [20 \cos(3000t) \text{ V}] [14.65 \cos(3000t + 46.94^\circ) \text{ mA}]$$

$$p_s(t) = 0.293 \cos(3000t) \cos(3000t + 46.94^\circ) \text{ W}$$

$$p_s(10 \text{ ms}) = 0.293 \cos(30) \cos(30 + 0.819) \text{ W} = 0.0374 \text{ W}$$

$$e_c(t) = (1/2) C v_c^2(t) = (1/2) (400 \text{ nF}) [20^2 \cos^2(3000t) \text{ V}^2]$$


$$e_c(10 \text{ ms}) = (1/2) (400 \text{ nF}) [400 \cos^2(30) \text{ V}^2] = 1.904 \text{ } \mu\text{J}$$

2. In the circuit below $R = 10 \text{ k}\Omega$, $L = 50 \text{ mH}$ and $C = 600 \text{ pF}$ with $\omega = 200,000 \text{ rad/s}$ and $I_{RC} = 1\angle 0^\circ \text{ A}$.

(a) Find the magnitude and angle of the phasor voltage V_C .

(b) Find the magnitude and angle of the phasor voltage V_L .

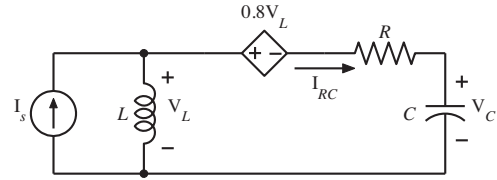(c) Find the magnitude and angle of the phasor current I_s .



$$V_C = I_{RC} \frac{1}{j\omega C} = (1\angle 0^\circ \text{ A}) \frac{1}{j(200,000 \text{ rad/s})(600 \times 10^{-12} \text{ F})} = -j8333 \text{ V} = 8,333\angle -90^\circ \text{ V}$$

$$-V_L + 0.8V_L + (1\angle 0^\circ \text{ A})(10,000 \Omega) + 8,333\angle -90^\circ \text{ V} = 0$$

$$-0.2V_L = (-10,000 - 8,333\angle -90^\circ) \text{ V} \Rightarrow V_L = \frac{-10,000 - 8,333\angle -90^\circ}{-0.2} \text{ V} = 65084\angle -39.8^\circ \text{ V}$$

$$I_L = \frac{V_L}{j\omega L} = \frac{65084\angle -39.8^\circ \text{ V}}{j(200,000 \text{ rad/s})(50 \text{ mH})} = 6.508\angle -129.8^\circ \text{ A} \text{ (flowing downward)}$$

$$I_s = I_{RC} + I_L = (1\angle 0^\circ + 6.508\angle -129.8^\circ) \text{ A} = 5.92\angle -122.35^\circ \text{ A}$$