

Solution of ECE 300 Test 10 S09

1. In the partial circuit below I is the phasor form of $i(t)$, I_C is the phasor form of $i_C(t)$ and V is the phasor form of $v(t)$. Find the numerical values of I_C and V in magnitude-angle form (angle in degrees).


$$\omega = 200$$

$$I_C = \frac{R}{R + 1/j\omega C} I = \frac{100}{100 + 1/(j200 \times 30 \times 10^{-6})} 3\angle 0^\circ = \frac{100}{100 - j166.67} 3\angle 0^\circ$$

$$I_C = \frac{100}{194.37\angle -59.04^\circ} 3\angle 0^\circ = 1.5434\angle 59.04^\circ$$

$$V = I_C \times 1/j\omega C = 1.5434\angle 59.04^\circ \times (166.67\angle -90^\circ) = 257.24\angle -30.96^\circ$$
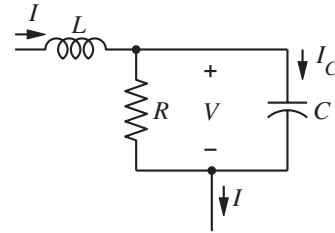
$$i(t) = 3\cos(200t) \text{ , } R = 100\Omega \text{ , } C = 30\mu\text{F}$$



2. In each part below find which current or voltage is leading the other and by how many degrees. The angle you report should be a positive angle between 0° and 180° .

(a) $v_1(t) = -4\cos(50t - 30^\circ)$, $v_2(t) = 3\sin(50t)$

$$v_1(t) = 4\cos(50t + 150^\circ) \text{ , } v_2(t) = 3\cos(50t - 90^\circ)$$

The phase-angle difference is $150^\circ - (-90^\circ) = 240^\circ > 180^\circ$. An equivalent phase-angle difference is $240^\circ - 360^\circ = -120^\circ$. So v_1 leads v_2 by -120° or v_2 leads v_1 by $+120^\circ$.

(b) $i_1(t) = 8\cos(2000t + 100^\circ)$, $i_2(t) = -3\sin(2000t + 20^\circ)$

$$i_1(t) = 8\cos(2000t + 100^\circ) \text{ , } i_2(t) = 3\sin(2000t - 160^\circ)$$

$$i_1(t) = 8\cos(2000t + 100^\circ) \text{ , } i_2(t) = 3\cos(2000t - 250^\circ)$$

The phase-angle difference is $100^\circ - (-250^\circ) = 350^\circ > 180^\circ$. An equivalent phase-angle difference is $350^\circ - 360^\circ = -10^\circ$. So i_1 leads i_2 by -10° or i_2 leads i_1 by $+10^\circ$.

Solution of ECE 300 Test 10 S09

1. In the partial circuit below I is the phasor form of $i(t)$, I_C is the phasor form of $i_C(t)$ and V is the phasor form of $v(t)$. Find the numerical values of I_C and V in magnitude-angle form (angle in degrees).


$$\omega = 100$$

$$I_C = \frac{R}{R + 1/j\omega C} I = \frac{100}{100 + 1/(j100 \times 30 \times 10^{-6})} 3\angle 0^\circ = \frac{100}{100 - j333.33} 3\angle 0^\circ$$

$$I_C = \frac{100}{348.007\angle -73.3^\circ} 3\angle 0^\circ = 0.8621\angle 73.3^\circ$$

$$V = I_C \times 1/j\omega C = 0.8621\angle 73.3^\circ \times (333.33\angle -90^\circ) = 287.36\angle -16.7^\circ$$
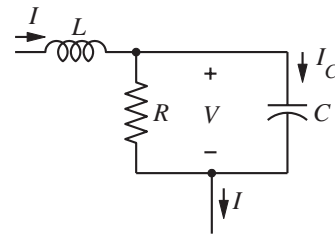
$$i(t) = 3\cos(100t), \quad R = 100\Omega, \quad C = 30\mu\text{F}$$



2. In each part below find which current or voltage is leading the other and by how many degrees. The angle you report should be a positive angle between 0° and 180° .

(a) $v_1(t) = -4\cos(50t - 80^\circ)$, $v_2(t) = 3\sin(50t)$

$$v_1(t) = 4\cos(50t + 100^\circ), \quad v_2(t) = 3\cos(50t - 90^\circ)$$

The phase-angle difference is $100^\circ - (-90^\circ) = 190^\circ > 180^\circ$. An equivalent phase-angle difference is $190^\circ - 360^\circ = -170^\circ$. So v_1 leads v_2 by -170° or v_2 leads v_1 by $+170^\circ$.

(b) $i_1(t) = 8\cos(2000t + 100^\circ)$, $i_2(t) = -3\sin(2000t - 50^\circ)$

$$i_1(t) = 8\cos(2000t + 100^\circ), \quad i_2(t) = 3\sin(2000t + 130^\circ)$$

$$i_1(t) = 8\cos(2000t + 100^\circ), \quad i_2(t) = 3\cos(2000t + 40^\circ)$$

The phase-angle difference is $100^\circ - 40^\circ = 60^\circ$. So i_1 leads i_2 by 60° .

Solution of ECE 300 Test 10 S09

1. In the partial circuit below I is the phasor form of $i(t)$, I_C is the phasor form of $i_C(t)$ and V is the phasor form of $v(t)$. Find the numerical values of I_C and V in magnitude-angle form (angle in degrees).


$$\omega = 300$$

$$I_C = \frac{R}{R + 1/j\omega C} I = \frac{100}{100 + 1/(j300 \times 30 \times 10^{-6})} 3\angle 0^\circ = \frac{100}{100 - j111.11} 3\angle 0^\circ$$

$$I_C = \frac{100}{149.48\angle -48.01^\circ} 3\angle 0^\circ = 2.007\angle 48.01^\circ$$

$$V = I_C \times 1/j\omega C = 2.007\angle 48.01^\circ \times (111.11\angle -90^\circ) = 223\angle -41.99^\circ$$
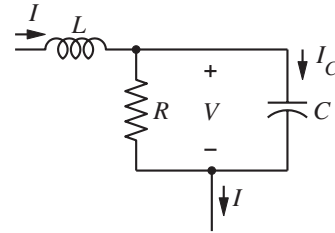
$$i(t) = 3\cos(300t) \text{ , } R = 100\Omega \text{ , } C = 30\mu\text{F}$$



2. In each part below find which current or voltage is leading the other and by how many degrees. The angle you report should be a positive angle between 0° and 180° .

(a) $v_1(t) = -4\cos(50t - 60^\circ)$, $v_2(t) = 3\sin(50t)$

$$v_1(t) = 4\cos(50t + 120^\circ) \text{ , } v_2(t) = 3\cos(50t - 90^\circ)$$

The phase-angle difference is $120^\circ - (-90^\circ) = 210^\circ > 180^\circ$. An equivalent phase-angle difference is $210^\circ - 360^\circ = -150^\circ$. So v_1 leads v_2 by -150° or v_2 leads v_1 by $+150^\circ$.

(b) $i_1(t) = 8\cos(2000t + 100^\circ)$, $i_2(t) = -3\sin(2000t + 70^\circ)$

$$i_1(t) = 8\cos(2000t + 100^\circ) \text{ , } i_2(t) = 3\sin(2000t - 110^\circ)$$

$$i_1(t) = 8\cos(2000t + 100^\circ) \text{ , } i_2(t) = 3\cos(2000t - 200^\circ)$$

The phase-angle difference is $100^\circ - (-200^\circ) = 300^\circ > 180^\circ$. An equivalent phase-angle difference is $300^\circ - 360^\circ = -60^\circ$. So i_1 leads i_2 by -60° or i_2 leads i_1 by $+60^\circ$.