

# Solution of ECE 300 Test 11 S09

1. (a) At a frequency of  $\omega = 1000$  rad/s, find the numerical magnitude and angle of the input impedance  $Z_{in}$  of the circuit below.

$$Z_{c1} = 1 / j\omega C_1 = -j50\Omega, \quad Z_{c2} = 1 / j\omega C_2 = -j200\Omega, \quad Z_L = j\omega L = j100\Omega$$

$$Z_{in} = (j100 - j200) \parallel 80 - j50 = \frac{-j8000}{80 - j100} - j50 = 101.513 \angle -61.28^\circ$$


- (b) There is a positive value of  $\omega$  at which the real part of the input impedance is zero. Find that numerical value of  $\omega$ .

$$Z_{in} = (j0.1\omega - j2 \times 10^5 / \omega) \parallel 80 - j5 \times 10^4 / \omega$$

If  $j0.1\omega - j2 \times 10^5 / \omega = 0$ , then the real part of  $Z_{in}$  will be zero.

Solving for  $\omega$  we get  $\omega = 1414.2$  rad/s.


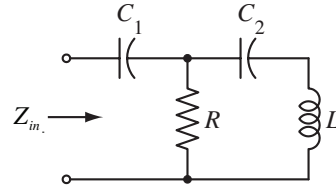
$$C_1 = 20\mu\text{F}, \quad C_2 = 5\mu\text{F}, \quad R = 80\Omega, \quad L = 100\text{mH}$$



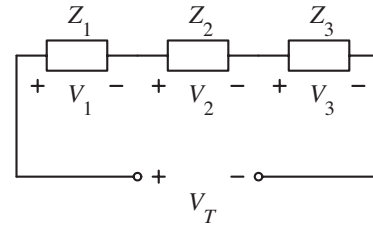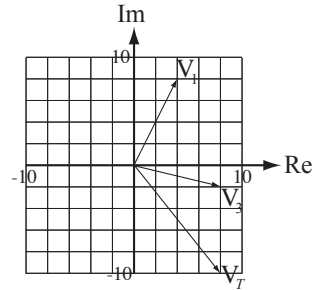2. With reference to the circuit and the phasor diagram below, find the numerical magnitude and angle of  $V_2$ .

$$V_1 = 4 + j8, V_3 = 8 - j2, V_T = 8 - j10$$

$$V_2 = V_T - V_1 - V_3 = 8 - j10 - (4 + j8) - (8 - j2) = -4 - j16 = 16.492 \angle -104.04^\circ$$



## Solution of ECE 300 Test 11 S09

1. (a) At a frequency of  $\omega = 1000$  rad/s, find the numerical magnitude and angle of the input impedance  $Z_{in}$  of the circuit below.

$$Z_{c1} = 1 / j\omega C_1 = -j50\Omega, \quad Z_{c2} = 1 / j\omega C_2 = -j200\Omega, \quad Z_L = j\omega L = j50\Omega$$

$$Z_{in} = (j50 - j200) \parallel 80 - j50 = \frac{-j12000}{80 - j150} - j50 = 103.945 \angle -53.19^\circ$$


- (b) There is a positive value of  $\omega$  at which the real part of the input impedance is zero. Find that numerical value of  $\omega$ .

$$Z_{in} = (j0.05\omega - j2 \times 10^5 / \omega) \parallel 80 - j5 \times 10^4 / \omega$$

If  $j0.05\omega - j2 \times 10^5 / \omega = 0$ , then the real part of  $Z_{in}$  will be zero.

Solving for  $\omega$  we get  $\omega = 2000$  rad/s.


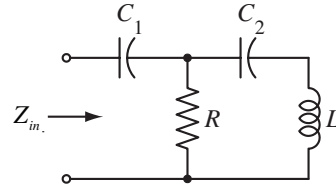
$$C_1 = 20\mu\text{F}, \quad C_2 = 5\mu\text{F}, \quad R = 80\Omega, \quad L = 50\text{mH}$$



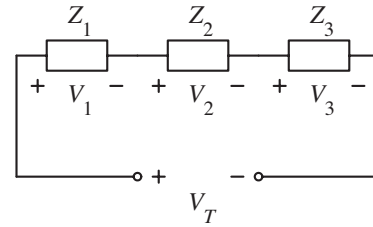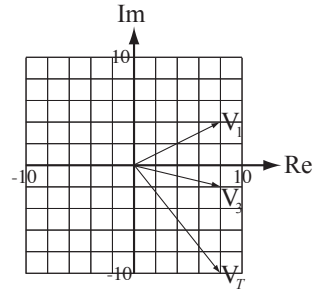2. With reference to the circuit and the phasor diagram below, find the numerical magnitude and angle of  $V_2$ .

$$V_1 = 8 + j4, V_3 = 8 - j2, V_T = 8 - j10$$

$$V_2 = V_T - V_1 - V_3 = 8 - j10 - (8 + j4) - (8 - j2) = -8 - j12 = 14.422 \angle -123.69^\circ$$



## Solution of ECE 300 Test 11 S09

1. (a) At a frequency of  $\omega = 1000 \text{ rad/s}$ , find the numerical magnitude and angle of the input impedance  $Z_{in}$  of the circuit below.

$$Z_{C1} = 1 / j\omega C_1 = -j50\Omega, \quad Z_{C2} = 1 / j\omega C_2 = -j200\Omega, \quad Z_L = j\omega L = j80\Omega$$

$$Z_{in} = (j80 - j200) \parallel 80 - j50 = \frac{-j9600}{80 - j120} - j50 = 103.07 \angle -57.5^\circ$$


- (b) There is a positive value of  $\omega$  at which the real part of the input impedance is zero. Find that numerical value of  $\omega$ .

$$Z_{in} = (j0.08\omega - j2 \times 10^5 / \omega) \parallel 80 - j5 \times 10^4 / \omega$$

If  $j0.08\omega - j2 \times 10^5 / \omega = 0$ , then the real part of  $Z_{in}$  will be zero.

Solving for  $\omega$  we get  $\omega = 1581.1 \text{ rad/s}$ .
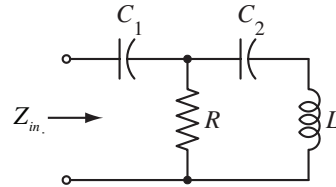
$$C_1 = 20\mu\text{F}, \quad C_2 = 5\mu\text{F}, \quad R = 80\Omega, \quad L = 80\text{mH}$$



2. With reference to the circuit and the phasor diagram below, find the numerical magnitude and angle of  $V_2$ .

$$V_1 = 8 + j4, V_3 = 2 + j8, V_T = 8 - j10$$

$$V_2 = V_T - V_1 - V_3 = 8 - j10 - (8 + j4) - (2 + j8) = -2 - j22 = 22.091 \angle -95.19^\circ$$

