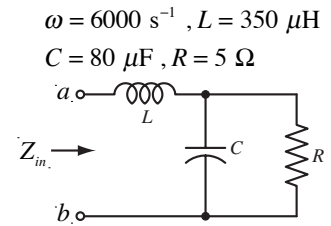


## Solution of ECE 202 Test 2 S13

1. (2 pts) Find the numerical magnitude and angle (in degrees) of the input impedance between terminals  $a$  and  $b$  in the partial circuit below.

$$Z_{in} = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^{\circ} \Omega$$



$$Z_{in} = \frac{R / j\omega C}{R + 1 / j\omega C} + j\omega L = \frac{R}{j\omega RC + 1} + j\omega L$$

$$Z_{in} = \frac{5}{j6000 \times 5 \times 80 \times 10^{-6} + 1} + j6000 \times 350 \times 10^{-6} = 0.808 \angle 23.711^{\circ}$$

2. (a) Find the numerical magnitudes and angles of the phasor voltages  $V_R$ ,  $V_L$  and  $V_C$  in the circuit below. (Be sure to check that  $V_s = V_R + V_L + V_C$ .)

$$V_R = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V} \quad V_L = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_R = \frac{R}{R + j\omega L + 1/j\omega C} V_s = \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_L = \frac{j\omega L}{R + j\omega L + 1/j\omega C} V_s = \frac{-\omega^2 LC}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_C = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} V_s = \frac{1}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_R = \frac{j200 \times 280 \times 20 \times 10^{-6}}{j200 \times 280 \times 20 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 20 \times 10^{-6}} 120 \angle 0^\circ = 114.24 \angle 17.829^\circ$$

$$V_L = \frac{-(200)^2 \times 0.8 \times 20 \times 10^{-6}}{j200 \times 280 \times 20 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 20 \times 10^{-6}} 120 \angle 0^\circ = 65.282 \angle 107.82^\circ$$

$$V_C = \frac{1}{j200 \times 280 \times 20 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 20 \times 10^{-6}} 120 \angle 0^\circ = 102.00 \angle -72.18^\circ$$

- (b) Find a new positive radian frequency  $\omega$  at which  $V_R = V_s$ .

$$\text{New } \omega = \underline{\hspace{2cm}} \text{ s}^{-1}$$

$$V_R = \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} V_s \Rightarrow \text{Choose } \omega^2 LC = 1 \Rightarrow \omega = \frac{1}{\sqrt{LC}} = 250$$

- (c) At the new radian frequency found in part (b) find the new numerical magnitudes and angles of the phasor voltages across the inductor and capacitor.


$$V_L = \frac{-(250)^2 \times 0.8 \times 20 \times 10^{-6}}{j250 \times 280 \times 20 \times 10^{-6} + 1 - (250)^2 \times 0.8 \times 20 \times 10^{-6}} 120 \angle 0^\circ = 85.714 \angle 90^\circ$$

$$V_C = \frac{1}{j250 \times 280 \times 20 \times 10^{-6} + 1 - (250)^2 \times 0.8 \times 20 \times 10^{-6}} 120 \angle 0^\circ = 85.714 \angle -90^\circ$$

$$V_L = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V} \quad V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_s = 120 \angle 0^\circ, R = 280 \Omega, L = 800 \text{mH}$$

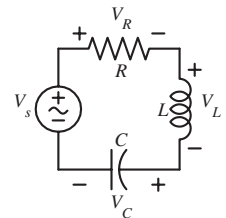
$$C = 20 \mu\text{F}, \omega = 200 \text{ s}^{-1}$$



## Solution of ECE 202 Test 2 S13

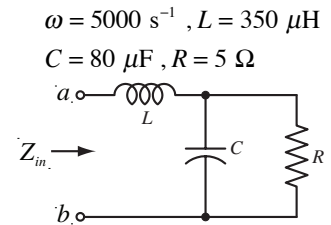1. (2 pts) Find the numerical magnitude and angle (in degrees) of the input impedance between terminals  $a$  and  $b$  in the partial circuit below.

$$Z_{in} = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^{\circ} \Omega$$



$$Z_{in} = \frac{R / j\omega C}{R + 1 / j\omega C} + j\omega L = \frac{R}{j\omega RC + 1} + j\omega L$$

$$Z_{in} = \frac{5}{j5000 \times 5 \times 80 \times 10^{-6} + 1} + j5000 \times 350 \times 10^{-6} = 1.0308 \angle -14.036^{\circ}$$

2. (a) Find the numerical magnitudes and angles of the phasor voltages  $V_R$ ,  $V_L$  and  $V_C$  in the circuit below. (Be sure to check that  $V_s = V_R + V_L + V_C$ .)

$$V_R = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V} \quad V_L = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_R = \frac{R}{R + j\omega L + 1/j\omega C} V_s = \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_L = \frac{j\omega L}{R + j\omega L + 1/j\omega C} V_s = \frac{-\omega^2 LC}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_C = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} V_s = \frac{1}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_R = \frac{j200 \times 280 \times 15 \times 10^{-6}}{j200 \times 280 \times 15 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 15 \times 10^{-6}} 120 \angle 0^\circ = 102.032 \angle 31.76^\circ$$

$$V_L = \frac{-(200)^2 \times 0.8 \times 15 \times 10^{-6}}{j200 \times 280 \times 15 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 15 \times 10^{-6}} 120 \angle 0^\circ = 58.304 \angle 121.76^\circ$$

$$V_C = \frac{1}{j200 \times 280 \times 15 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 15 \times 10^{-6}} 120 \angle 0^\circ = 121.4664 \angle -58.241^\circ$$

- (b) Find a new positive radian frequency  $\omega$  at which  $V_R = V_s$ .

$$\text{New } \omega = \underline{\hspace{2cm}} \text{ s}^{-1}$$

$$V_R = \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} V_s \Rightarrow \text{Choose } \omega^2 LC = 1 \Rightarrow \omega = \frac{1}{\sqrt{LC}} = 288.68$$

- (c) At the new radian frequency found in part (b) find the new numerical magnitudes and angles of the phasor voltages across the inductor and capacitor.


$$V_L = \frac{-(288.68)^2 \times 0.8 \times 20 \times 10^{-6}}{j288.68 \times 280 \times 15 \times 10^{-6} + 1 - (288.68)^2 \times 0.8 \times 15 \times 10^{-6}} 120 \angle 0^\circ = 98.98 \angle 90^\circ$$

$$V_C = \frac{1}{j288.68 \times 280 \times 15 \times 10^{-6} + 1 - (288.68)^2 \times 0.8 \times 15 \times 10^{-6}} 120 \angle 0^\circ = 98.98 \angle -90^\circ$$

$$V_L = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V} \quad V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_s = 120 \angle 0^\circ, R = 280 \Omega, L = 800 \text{mH}$$

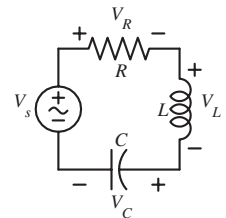
$$C = 15 \mu\text{F}, \omega = 200 \text{ s}^{-1}$$



## Solution of ECE 202 Test 2 S13

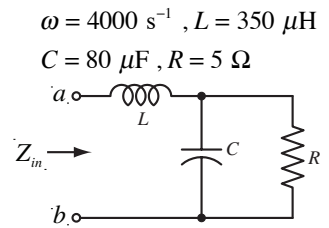1. (2 pts) Find the numerical magnitude and angle (in degrees) of the input impedance between terminals  $a$  and  $b$  in the partial circuit below.

$$Z_{in} = \text{_____} \angle \text{_____}^\circ \Omega$$



$$Z_{in} = \frac{R / j\omega C}{R + 1 / j\omega C} + j\omega L = \frac{R}{j\omega RC + 1} + j\omega L$$

$$Z_{in} = \frac{5}{j4000 \times 5 \times 80 \times 10^{-6} + 1} + j4000 \times 350 \times 10^{-6} = 1.6402 \angle -31.1^\circ$$

2. (a) Find the numerical magnitudes and angles of the phasor voltages  $V_R$ ,  $V_L$  and  $V_C$  in the circuit below. (Be sure to check that  $V_s = V_R + V_L + V_C$ .)

$$V_R = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V} \quad V_L = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_R = \frac{R}{R + j\omega L + 1/j\omega C} V_s = \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_L = \frac{j\omega L}{R + j\omega L + 1/j\omega C} V_s = \frac{-\omega^2 LC}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_C = \frac{1/j\omega C}{R + j\omega L + 1/j\omega C} V_s = \frac{1}{j\omega RC + 1 - \omega^2 LC} V_s$$

$$V_R = \frac{j200 \times 280 \times 25 \times 10^{-6}}{j200 \times 280 \times 25 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 25 \times 10^{-6}} 120 \angle 0^\circ = 118.794 \angle 8.13^\circ$$

$$V_L = \frac{-(200)^2 \times 0.8 \times 25 \times 10^{-6}}{j200 \times 280 \times 25 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 25 \times 10^{-6}} 120 \angle 0^\circ = 67.882 \angle 98.13^\circ$$

$$V_C = \frac{1}{j200 \times 280 \times 25 \times 10^{-6} + 1 - (200)^2 \times 0.8 \times 25 \times 10^{-6}} 120 \angle 0^\circ = 84.853 \angle -81.87^\circ$$

- (b) Find a new positive radian frequency  $\omega$  at which  $V_R = V_s$ .

$$\text{New } \omega = \underline{\hspace{2cm}} \text{ s}^{-1}$$

$$V_R = \frac{j\omega RC}{j\omega RC + 1 - \omega^2 LC} V_s \Rightarrow \text{Choose } \omega^2 LC = 1 \Rightarrow \omega = \frac{1}{\sqrt{LC}} = 223.607$$

- (c) At the new radian frequency found in part (b) find the new numerical magnitudes and angles of the phasor voltages across the inductor and capacitor.

$$V_L = \frac{-(223.607)^2 \times 0.8 \times 25 \times 10^{-6}}{j223.607 \times 280 \times 25 \times 10^{-6} + 1 - (223.607)^2 \times 0.8 \times 25 \times 10^{-6}} 120 \angle 0^\circ = 76.6653 \angle 90^\circ$$

$$V_C = \frac{1}{j223.607 \times 280 \times 25 \times 10^{-6} + 1 - (223.607)^2 \times 0.8 \times 25 \times 10^{-6}} 120 \angle 0^\circ = 76.665 \angle -90^\circ$$

$$V_L = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V} \quad V_C = \underline{\hspace{2cm}} \angle \underline{\hspace{2cm}}^\circ \text{V}$$

$$V_s = 120 \angle 0^\circ, R = 280 \Omega, L = 800 \text{mH} \\ C = 25 \mu\text{F}, \omega = 200 \text{ s}^{-1}$$

