

# Solution of ECE 315 Test 12 F05

1. For the transfer function  $\frac{V_o(j\omega)}{V_i(j\omega)}$ , at  $\omega = 30$  the magnitude Bode diagram passes through -10 dB. If  $|V_o(j30)| = K|V_i(j30)|$  what is the numerical value of  $K$ ?

$K = \underline{0.316}$

$$\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\text{dB}} = 20 \log_{10} \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| \Rightarrow \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = 10^{V_o(j\omega)/V_i(j\omega)_{\text{dB}}/20}$$

$$\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\text{dB}} = -10 \Rightarrow \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = 10^{(-10/20)} = 10^{-1/2} = \frac{1}{\sqrt{10}} = 0.316 \Rightarrow K = 0.316$$

2. In an inverting op-amp amplifier, the feedback component is a 1000  $\Omega$  resistor and the component between the input voltage terminal and the operational amplifier's inverting input is a 10  $\mu\text{F}$  capacitor. If the voltage transfer function is  $H(f)$ , what are the magnitude and phase of  $H(200)$ ?

$|H(200)| = \underline{12.57}$        $\angle H(200) = \underline{-\pi / 2 = -1.57}$

$$H(f) = -\frac{Z_f(f)}{Z_i(f)} = -\frac{R}{1/j2\pi fC} = -j2\pi fRC$$

$$H(200) = -j400\pi \times 1000 \times 10^{-5} = -j4\pi = -j12.57$$

$$|H(200)| = 12.57, \quad \angle H(200) = -\pi / 2 = -1.57$$

3. An active op-amp integrator has a transfer-function magnitude Bode diagram that goes through -40 dB at  $\omega = 500$ . At what numerical value of  $\omega$  is the system transfer function magnitude 100 times smaller than it is at  $\omega = 500$ ?  $\omega = \underline{50000}$

A factor-of-100 reduction in system transfer function magnitude is equivalent to a change of -40 dB. Since the Bode diagram passes through -40 dB at  $\omega = 500$ , we need to find the frequency at which the Bode diagram passes through -80 dB. The slope of the Bode diagram for any integrator is -20 dB/decade. Therefore if the diagram passes through -40 dB at  $\omega = 500$  it passes through -80 dB at  $\omega = 50000$ .

## Solution of ECE 315 Test 12 F05

1. For the transfer function  $\frac{V_o(j\omega)}{V_i(j\omega)}$ , at  $\omega = 30$  the magnitude Bode diagram passes through -15 dB. If  $|V_o(j30)| = K|V_i(j30)|$  what is the numerical value of  $K$ ?  
 $K = \underline{0.178}$

$$\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\text{dB}} = 20 \log_{10} \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| \Rightarrow \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = 10^{|V_o(j\omega)/V_i(j\omega)|_{\text{dB}}/20}$$

$$\left| \frac{V_o(j\omega)}{V_i(j\omega)} \right|_{\text{dB}} = -15 \Rightarrow \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = 10^{(-15/20)} = 10^{(-3/4)} = 0.178 \Rightarrow K = 0.178$$

2. In an inverting op-amp amplifier, the feedback component is a 1000  $\Omega$  resistor and the component between the input voltage terminal and the operational amplifier's inverting input is a 10  $\mu\text{F}$  capacitor. If the voltage transfer function is  $H(f)$ , what are the magnitude and phase of  $H(100)$ ?

$$|H(100)| = \underline{6.28} \qquad H(100) = \underline{-\pi / 2 = -1.57}$$

$$H(f) = -\frac{Z_f(f)}{Z_i(f)} = -\frac{R}{1/j2\pi fC} = -j2\pi fRC$$

$$H(200) = -j200\pi \times 1000 \times 10^{-5} = -j2\pi = -j6.28$$

$$|H(200)| = 6.28 \quad , \quad H(200) = -\pi / 2 = -1.57$$

3. An active differentiator has a transfer-function magnitude Bode diagram that goes through -40 dB at  $\omega = 500$ . At what numerical value of  $\omega$  is the system transfer function magnitude 100 times smaller than it is at  $\omega = 500$ ?  $\omega = \underline{5}$

A factor-of-100 reduction in system transfer function magnitude is equivalent to a change of -40 dB. Since the Bode diagram passes through -40 dB at  $\omega = 500$ , we need to find the frequency at which the Bode diagram passes through -80 dB. The

slope of the Bodediagram for any integrator is +20 dB/decade. Therefore if the diagram passes through -40 dB at  $\omega = 500$  it passes through -80 dB at  $\omega = 5$ .