

# Solution of ECE 315 Test 13 F04

1. An LTI system has a transfer function,

$$H(j\omega) = \frac{j3\omega - \omega^2}{1000 - 10\omega^2 + j250\omega}.$$

(a) Find all the corner frequencies (in radians per second) in a magnitude Bode plot of this transfer function.

Corner frequencies (radians/s): 3, 5, 20 (and 0)

Corner frequencies are the magnitudes of the locations of the non-zero real poles and zeros and the radian resonant frequencies of any complex poles or zeros.

$$H(j\omega) = \frac{j\omega(j\omega + 3)}{10(j\omega)^2 + j250\omega + 1000} = \frac{1}{10} \times j\omega \times (j\omega + 3) \times \frac{1}{(j\omega + 5)(j\omega + 20)}$$


Zeros at  $j\omega = 0$  and  $j\omega = -3$ . Poles at  $j\omega = -5$  and  $j\omega = -20$ . (There is not actually a “corner” at zero but I accepted it anyway.)

(b) At very low and very high frequencies what is the slope of the magnitude Bode plot in dB/decade?

Slope = +20 dB/decade at very low frequencies and 0 dB/decade at very high frequencies

At very low frequencies the transfer function is approximately  $H(j\omega) = j3\omega / 1000$ . This is a frequency-independent gain times a single differentiator so the slope is +20 dB/decade. At very high frequencies the transfer function is approximately  $H(j\omega) = \frac{j\omega(j\omega)}{10(j\omega)^2} = \frac{1}{10}$  which is a constant so the slope is 0 dB/decade.

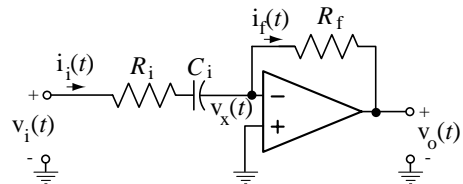2. (a) Find the transfer function,  $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$ , of this active filter with  $R_i = 1000 \Omega$ ,  $C_i = 1\mu\text{F}$  and  $R_f = 5000 \Omega$ .



Using the gain formula for an inverting amplifier,  $H(j\omega) = -\frac{R_f}{R_i + \frac{1}{j\omega C_i}} = -\frac{j\omega R_f C_i}{j\omega R_i C_i + 1} = -\frac{j5 \times 10^{-3} \omega}{j10^{-3} \omega + 1}$ .

(b) Find all the corner frequencies (in radians per second) in a magnitude Bode plot of this transfer function.

Corner frequencies (radians/s): 1000 (and 0)

There is one real pole at  $j10^{-3}\omega + 1 = 0 \Rightarrow j\omega = -1000$  and one real zero at  $j\omega = 0$ . (Again, there is not actually a “corner” at zero but I accepted it anyway.)

(c) At very low and very high frequencies what is the slope of the magnitude Bode plot in dB/decade?

Slope = +20 dB/decade at very low frequencies and 0 dB/decade at very high frequencies

At very low frequencies the transfer function is approximately  $H(j\omega) = -j5 \times 10^{-3} \omega$ . This is a single differentiator times a frequency-independent gain of  $-5 \times 10^{-3}$  so the slope is +20 dB/decade. At very high frequencies the transfer function is approximately  $H(j\omega) = -5$  which is a constant so the slope is 0 dB/decade.

# Solution of ECE 315 Test 13 F04

1. An LTI system has a transfer function,

$$H(j\omega) = \frac{1200 - 10\omega^2 + j340\omega}{j6\omega - \omega^2}.$$

(a) Find all the corner frequencies (in radians per second) in a magnitude Bode plot of this transfer function.

Corner frequencies (radians/s): 6, 4, 30 (and 0)

Corner frequencies are the magnitudes of the locations of the non-zero real poles and zeros and the radian resonant frequencies of any complex poles or zeros.

$$H(j\omega) = \frac{10(j\omega)^2 + j340\omega + 1200}{j\omega(j\omega + 6)} = 10 \times (j\omega + 4)(j\omega + 30) \times \frac{1}{j\omega} \times \frac{1}{j\omega + 6}$$


Zeros at  $j\omega = -4$  and  $j\omega = -30$ . Poles at  $j\omega = 0$  and  $j\omega = -6$ . (There is not actually a “corner” at zero but I accepted it anyway.)

(b) At very low and very high frequencies what is the slope of the magnitude Bode plot in dB/decade?

Slope = -20 dB/decade at very low frequencies and 0 dB/decade at very high frequencies

At very low frequencies the transfer function is approximately  $H(j\omega) = 200 / j\omega$ . This is a frequency-independent gain times a single integrator so the slope is -20 dB/decade. At very high frequencies the transfer function is approximately  $H(j\omega) = 10$  which is a constant so the slope is 0 dB/decade.

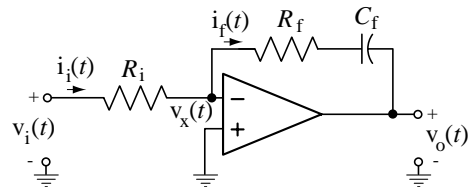2. (a) Find the transfer function,  $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$ , of this active filter with  $R_i = 2000 \Omega$ ,  $C_f = 1\mu\text{F}$  and  $R_f = 4000 \Omega$ .



$$\text{Using the gain formula for an inverting amplifier, } H(j\omega) = -\frac{R_f + \frac{1}{j\omega C_f}}{R_i} = -\frac{j\omega R_f C_f + 1}{j\omega R_i C_f} = -\frac{j4 \times 10^{-3} \omega + 1}{j2 \times 10^{-3} \omega}.$$

(b) Find all the corner frequencies (in radians per second) in a magnitude Bode plot of this transfer function.

Corner frequencies (radians/s): 250 (and 0)

There is one real zero at  $j4 \times 10^{-3} \omega + 1 = 0 \Rightarrow j\omega = -250$  and one real pole at  $j\omega = 0$ . (Again, there is not actually a “corner” at zero but I accepted it anyway.)

(c) At very low and very high frequencies what is the slope of the magnitude Bode plot in dB/decade?

Slope = -20 dB/decade at very low frequencies and 0 dB/decade at very high frequencies

At very low frequencies the transfer function is approximately  $H(j\omega) = -500 / j\omega$ . This is a single integrator times a frequency-independent gain of  $-500$  so the slope is  $-20$  dB/decade. At very high frequencies the transfer function is approximately  $H(j\omega) = -2$  which is a constant so the slope is  $0$  dB/decade.