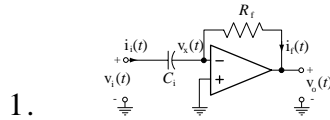




Solution to ECE Test #13 F03

In the active filters below all resistors are 1 ohm and all capacitors are 1 farad. For each filter the transfer function is $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$. Identify the transfer-function magnitude Bode diagram for each circuit by entering the correct letter.



$|H(j\omega)|$ is $\left| \frac{R_f}{1} \right|$. At very low frequencies that ratio approaches zero (negative infinity in dB) and at very high frequencies it approaches infinity (positive infinity in dB).

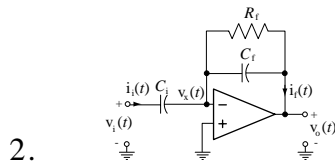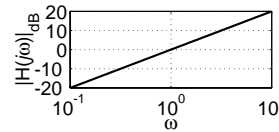
$$H(j\omega) = -\frac{R_f}{1} = -j\omega R_f C_i \Rightarrow \text{Differentiator}$$




At very low frequencies $|H(j\omega)|$ is $\left| \frac{R_f}{1} \right|$ which approaches zero (negative infinity in dB).

At very high frequencies it is $\left| \frac{1}{j\omega C_f} \right|$ which is $\frac{C_i}{C_f} = 1$ or 0 dB.
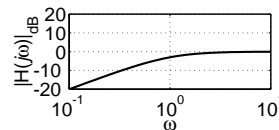
$$H(j\omega) = -\frac{R_f \frac{1}{j\omega C_f}}{R_f + \frac{1}{j\omega C_f}} = -\frac{j\omega R_f C_i}{j\omega R_f C_f + 1} \Rightarrow \text{Highpass Filter}$$




3.

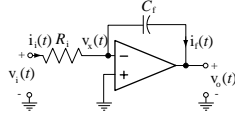


$|H(j\omega)|$ is $\left| \frac{1}{\frac{j\omega C_f}{R_i}} \right|$. At very low frequencies that ratio approaches infinity (positive infinity in dB) and at very high frequencies it approaches zero (negative infinity in dB).
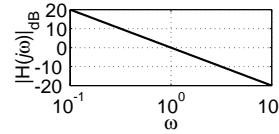
$$H(j\omega) = -\frac{1}{\frac{j\omega C_f}{R_i}} = -\frac{1}{j\omega R_i C_f} \Rightarrow \text{Integrator}$$




4.

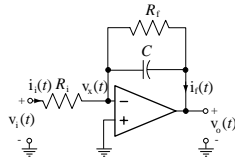


At very low frequencies $|H(j\omega)|$ approaches $\frac{R_f}{R_i} = 1$ or 0 dB. At very high frequencies it

approaches $\left| \frac{1}{\frac{j\omega C}{R_i}} \right| = 0$, (negative infinity in dB).
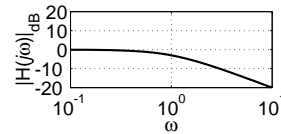
$$H(j\omega) = -\frac{R_f \frac{1}{j\omega C}}{R_i + \frac{1}{j\omega C}} = -\frac{R_f}{R_i} \frac{1}{j\omega R_f C + 1} \Rightarrow \text{Lowpass Filter}$$




5.

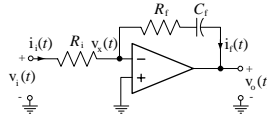


At very low frequencies $|H(j\omega)|$ approaches $\left| \frac{1}{\frac{j\omega C_f}{R_i}} \right|$ which approaches infinity (positive infinity in dB). At very high frequencies it approaches $\frac{R_f}{R_i} = 1$ or 0 dB.
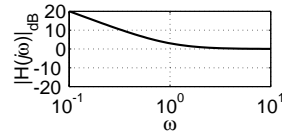
$$H(j\omega) = -\frac{R_f + \frac{1}{j\omega C_f}}{R_i} = -\frac{j\omega R_f C_f + 1}{j\omega R_i C_f}$$




6.

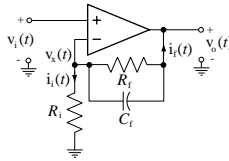


At very low frequencies $|H(j\omega)|$ approaches $\frac{R_f + R_i}{R_i} = 2$ or 6 dB. At very high frequencies it approaches $\frac{R_f}{R_i} = 1$ or 0 dB.

frequencies it approaches $\left| \frac{\frac{1}{j\omega C_f} + R_i}{R_i} \right| = 1$ or 0 dB.
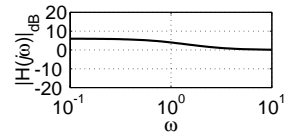
$$H(j\omega) = \frac{\frac{R_f}{j\omega C_f} + R_i}{R_i + \frac{1}{j\omega C_f}} = \frac{j\omega R_i R_f C_f + (R_i + R_f)}{j\omega R_i R_f C_f + R_i}$$




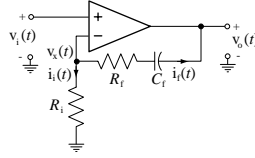


7.

At very low frequencies $|H(j\omega)|$ approaches $\left| \frac{1}{j\omega C_f} + R_i \right|$ which approaches infinity

(positive infinity in dB). At very high frequencies it approaches $\frac{R_f + R_i}{R_i} = 2$ or 6 dB.
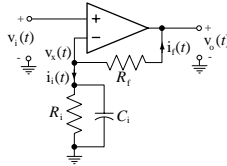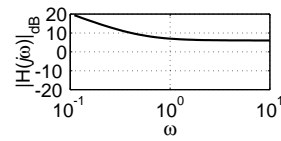
$$H(j\omega) = \frac{R_f + \frac{1}{j\omega C_f} + R_i}{R_i} = \frac{j\omega(R_f + R_i)C_f + 1}{j\omega R_i C_f}$$



8.

At very low frequencies $|H(j\omega)|$ approaches $\frac{R_f + R_i}{R_i} = 2$ or 6 dB. At very high

frequencies it approaches $\left| \frac{R_f + \frac{1}{j\omega C_i}}{\frac{1}{j\omega C_i}} \right|$ which approaches infinity (positive infinity in dB).

$$H(j\omega) = \frac{R_f + \frac{1}{j\omega C_i} R_i}{\frac{1}{j\omega C_i} + R_i} = \frac{j\omega R_f R_i C_i + R_i + R_f}{R_i}$$

