Sinusoidal Analysis (Ch 19)

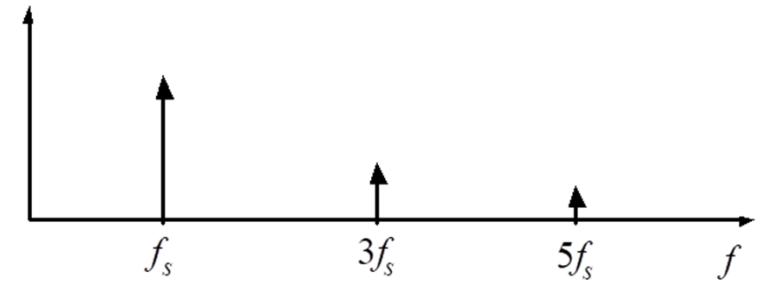

 

 

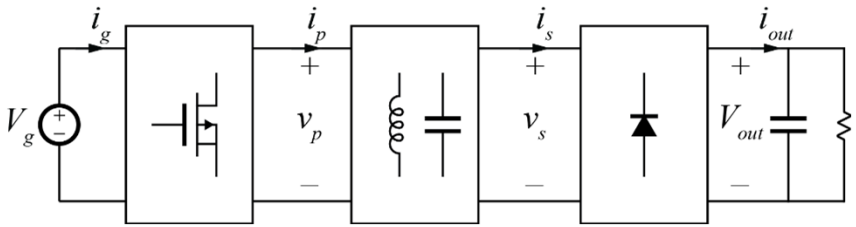

Sinusoidal Analysis: Comments

- Generally most accurate when operating near resonance with a high Q
- Effective quality factor Q_e depends not only on resonant tank, but also on loading
- Analysis neglects switching intervals; can only predict where ZVS **cannot** be obtained

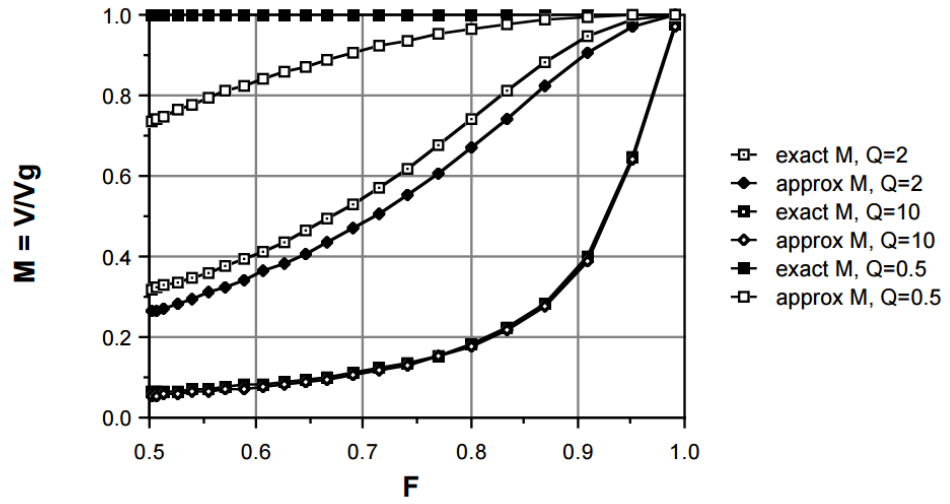

Fig. 2.14. Comparison of exact and approximate series resonant converter characteristics, below resonance.

AC Link Waveforms

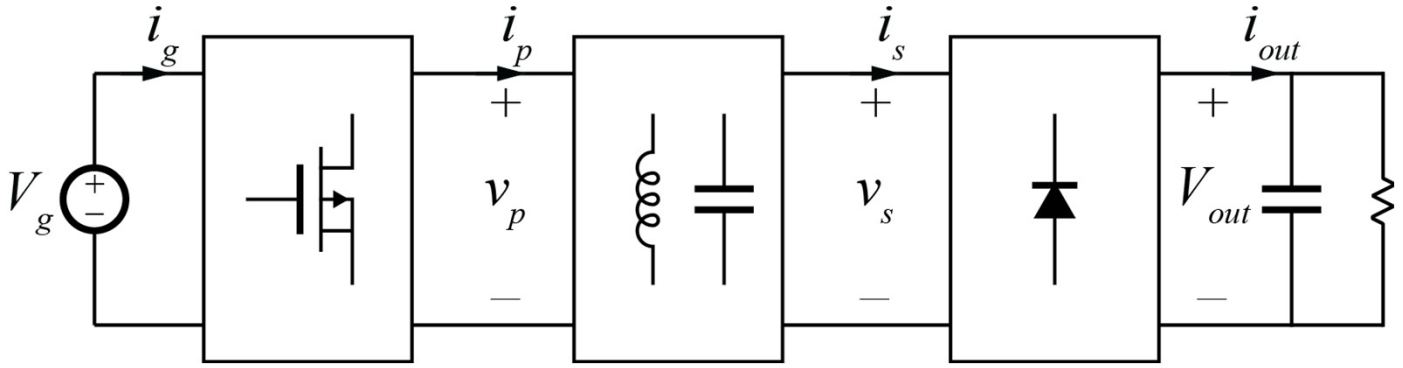

Switch Network Sinusoidal Analysis

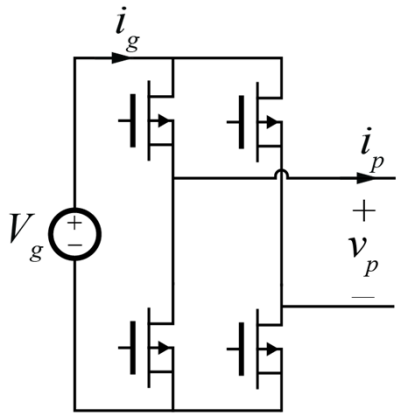

 

Input Current

Switch Network Equivalent Circuit

Diode Rectifier Sinusoidal Analysis

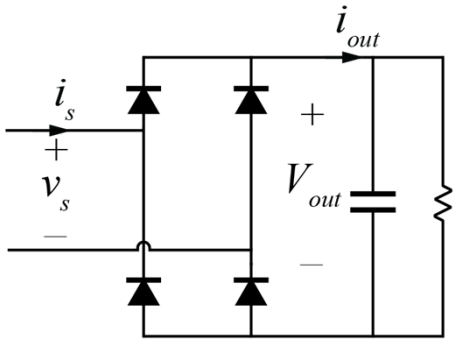

 

Diode Rectifier Equivalent Circuit

Other Implementations